
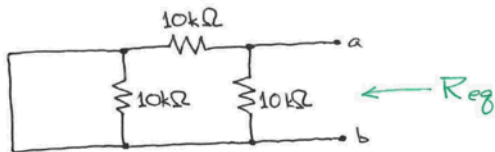


Since there are no dependent sources

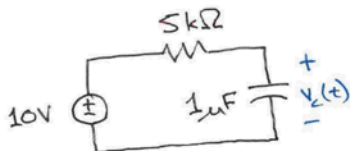

$$R_{eq} = 10k\Omega \parallel 10k\Omega = 5k\Omega$$

The Thevenin equivalent is then:



$$v_c(0) = 0$$

$$V_{oc} = 10V$$

$$\tau = RC = (5k\Omega)(1\mu F) = 5ms$$

From which:

$$v_c(t) = V_{oc} + [v_c(0) - V_{oc}] e^{-t/\tau}$$

$$= 10 + [0 - 10] e^{-t/0.005}$$

$$= \underline{\underline{10 - 10e^{-200t} V}}$$

$$i_c(t) = C \frac{dv_c(t)}{dt}$$

$$= 10^{-6} (-10) (-200) e^{-200t}$$

$$= \underline{\underline{2e^{-200t} \text{ mA}}}$$

$$\begin{aligned}
 P_c(t) &= v_c(t) i_c(t) \\
 &= (10 - 10e^{-200t})(2e^{-200t}) \\
 &= \underline{\underline{20e^{-200t} - 20e^{-400t} \text{ mW}}}
 \end{aligned}$$

$$\begin{aligned}
 w_c(t) &= \frac{1}{2} C v_c^2(t) \\
 &= \frac{1}{2} (10^{-6}) (10 - 10e^{-200t})^2 \\
 &= \underline{\underline{50 - 100e^{-200t} + 50e^{-400t} \text{ } \mu\text{J}}}
 \end{aligned}$$

Now determine the power absorbed by the resistors:

$$P_{R_1} = \frac{V_s^2}{R_1} = \frac{20^2}{10^4} = \underline{\underline{40 \text{ mW}}}$$

$$\begin{aligned}
 P_{R_2}(t) &= \frac{[V_s - v_c(t)]^2}{R_2} \\
 &= \frac{(10 + 10e^{-200t})^2}{10^4} \\
 &= \underline{\underline{10 + 20e^{-200t} + 10e^{-400t} \text{ mW}}}
 \end{aligned}$$

$$\begin{aligned}
 P_{R_3}(t) &= \frac{v_c^2(t)}{R_3} \\
 &= \frac{(10 - 10e^{-200t})^2}{10^4} \\
 &= \underline{\underline{10 - 20e^{-200t} + 10e^{-400t} \text{ mW}}}
 \end{aligned}$$

For the power supplied by the source:

$$\begin{aligned}P_{V_s}(t) &= P_{R_1} + P_{R_2}(t) + P_{R_3}(t) + P_C(t) \\&= \underline{\underline{60 + 20e^{-200t} \text{ mW}}}\end{aligned}$$

Finally at $t = 10 \text{ ms}$:

$$V_C = 8.647 \text{ V}$$

$$i_C = 270.6 \mu\text{A}$$

$$P_C = 2.340 \text{ mW (abs)}$$

$$P_{R_1} = 40 \text{ mW (abs)}$$

$$P_{R_2} = 12.89 \text{ mW (abs)}$$


$$P_{R_3} = 7.477 \text{ mW (abs)}$$

$$P_{V_s} = 62.71 \text{ mW (sup)}$$


$$W_C = 37.39 \mu\text{J}$$

$$\text{Note: } \sum P_{\text{sup}} \overset{\checkmark}{=} \sum P_{\text{abs}}$$


C: Voltage

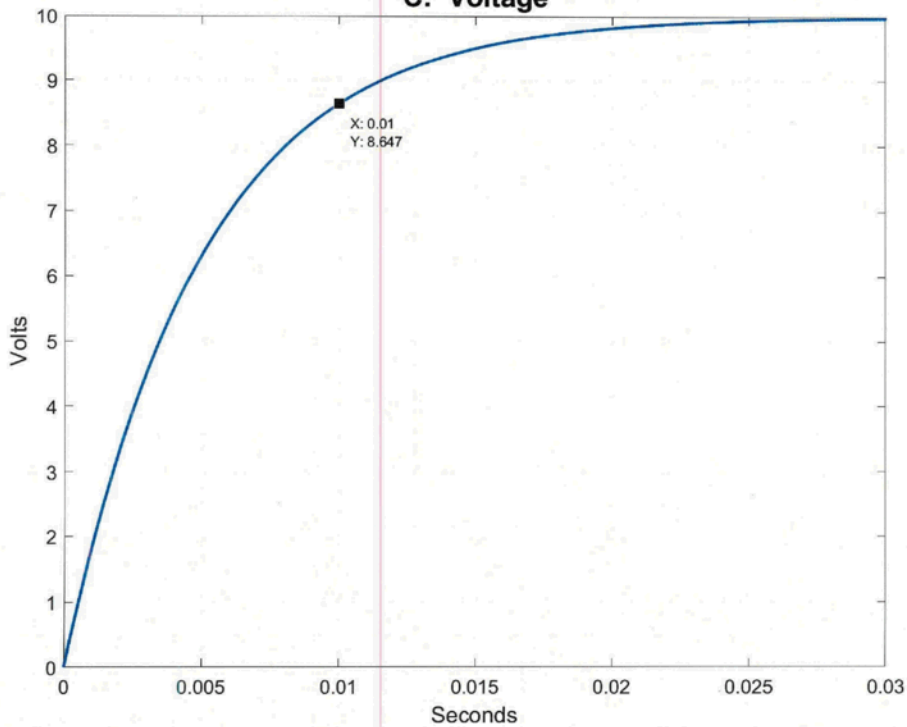


C: Current

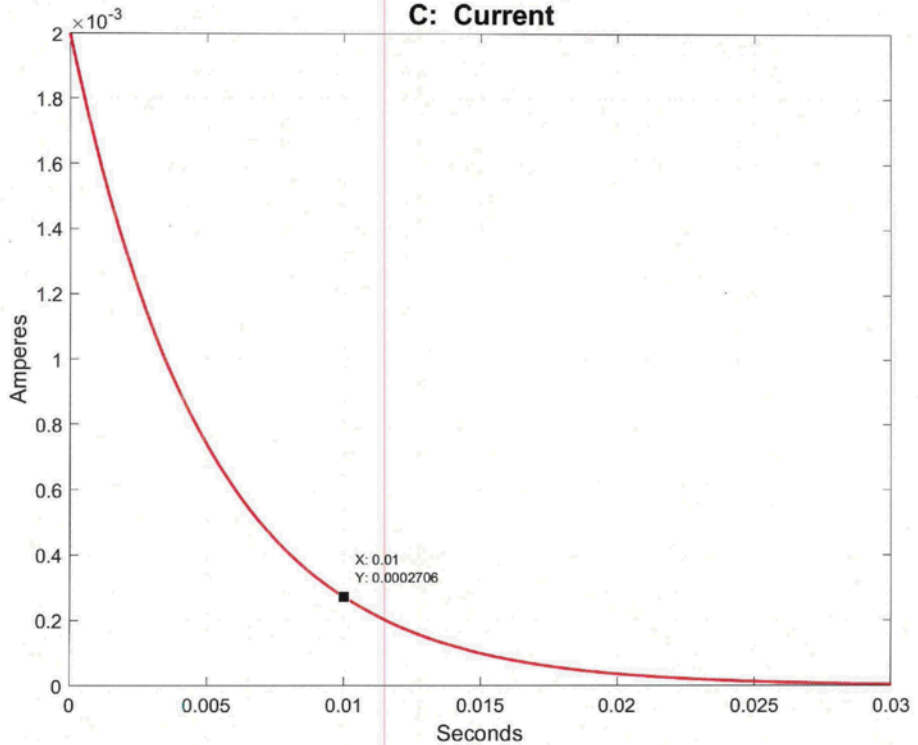


C: Power Absorbed

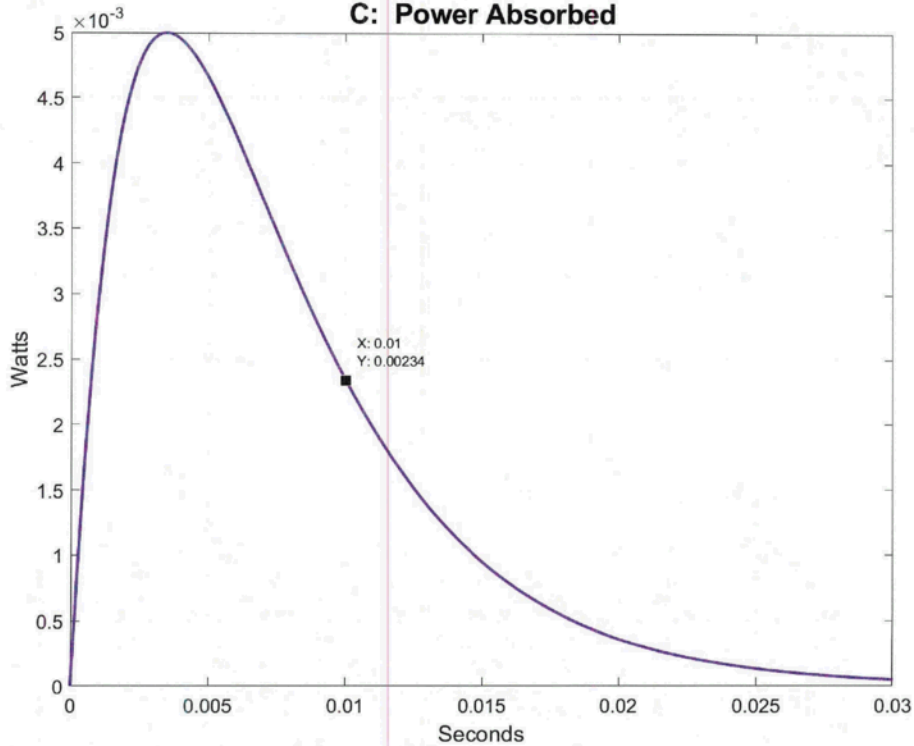


C: Energy Absorbed

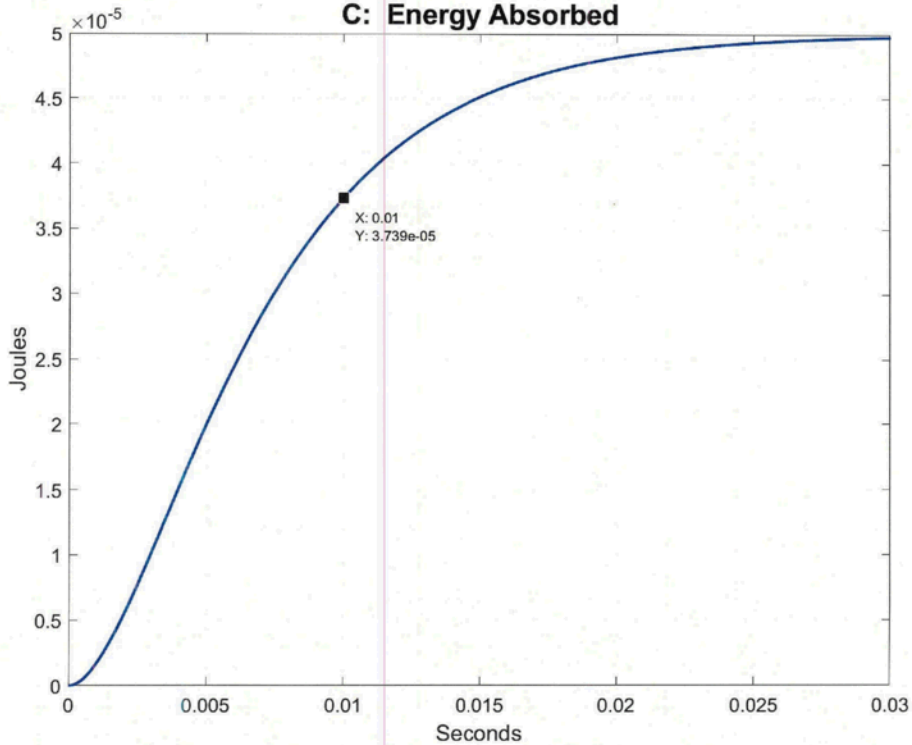

R1: Power Absorbed

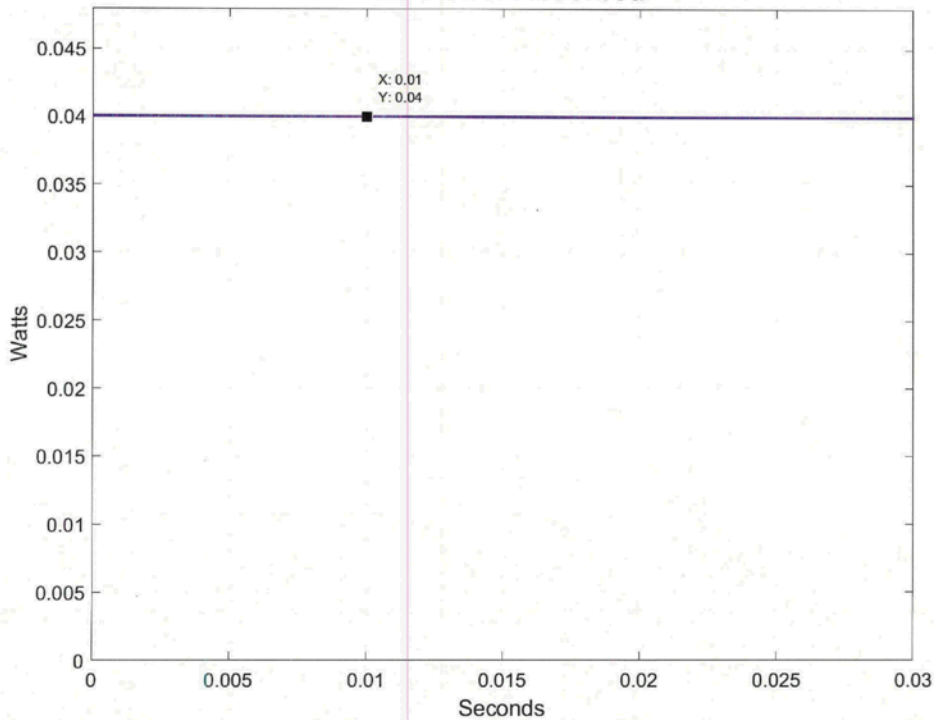

R2: Power Absorbed

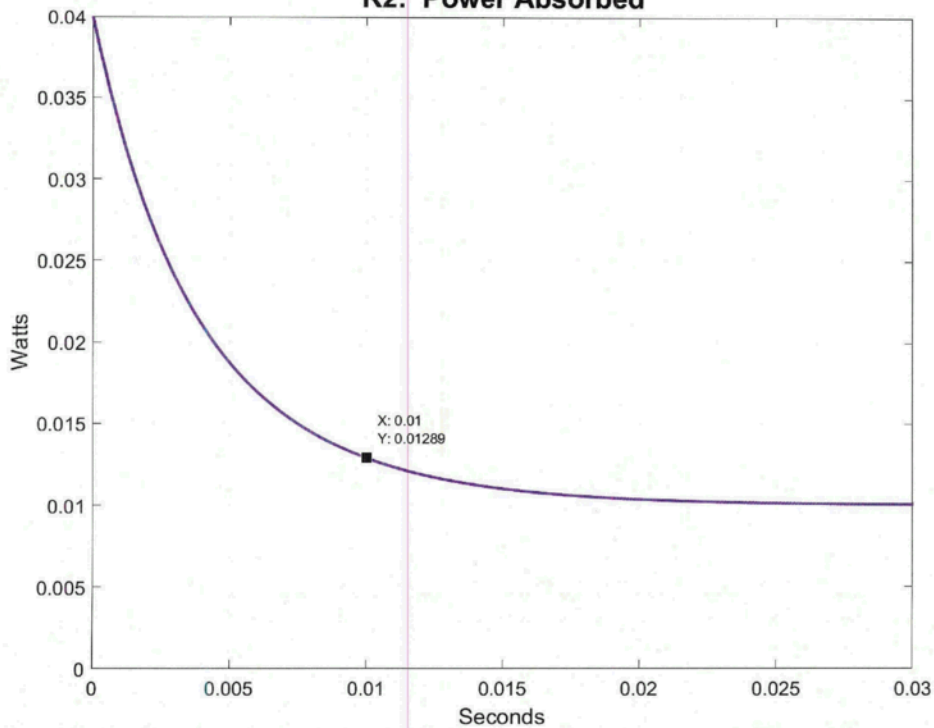

R3: Power Absorbed

