
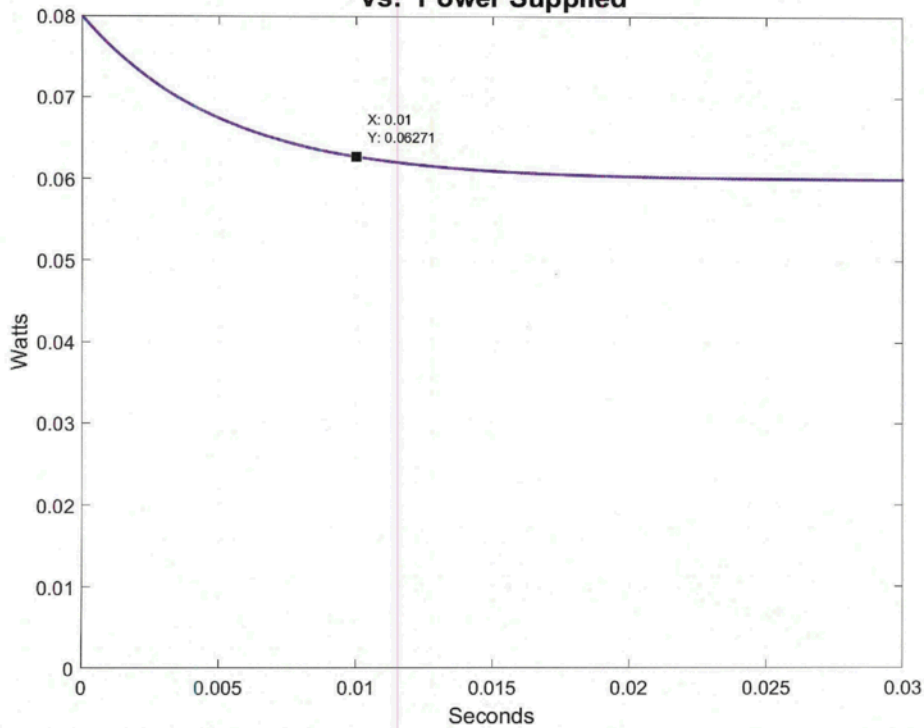


Vs: Power Supplied

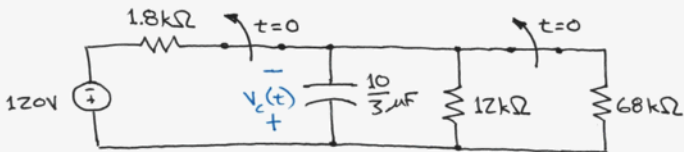

Problem 7.26



First find $v_c(t)$

$$v_c(0) = \frac{10.2}{1.8 + 10.2} (120) = 102 \text{ V}$$

$$V_{oc} = 0$$

$$\tau = RC = (12\text{k}\Omega) \left(\frac{10}{3} \mu\text{F} \right) = 40\text{ms}$$

$$\text{So, } \underline{\underline{v_c(t) = 102 e^{-25t} \text{ V}}}$$

$$a) P_{12k}(t) = \frac{v_c^2(t)}{12\text{k}\Omega} = 0.867 e^{-50t} \text{ W}$$

$$\begin{aligned} w_{12k}(t) &= \int_0^t P_{12k}(\tau) d\tau \\ &= \frac{0.867}{-50} e^{-50\tau} \bigg|_0^t \\ &= 17.34 (1 - e^{-50t}) \text{ mJ} \end{aligned}$$

$$\underline{\underline{w_{12k}(12\text{ms}) = 7.824 \text{ mJ}}}$$


$$\begin{aligned}
 b) \quad w_c(t) &= \frac{1}{2} C v_c^2(t) \\
 &= \frac{1}{2} \left(\frac{10}{3} \times 10^{-6} \right) (102)^2 e^{-50t} \\
 &= 17.34 e^{-50t} \text{ mJ}
 \end{aligned}$$

$$w_c(t_x) = (.25)(17.34) = 17.34 e^{-50t_x}$$

$$50, \quad -50t_x = \ln 0.25$$

$$t_x = \frac{\ln 0.25}{-50} = \underline{\underline{27.73 \text{ ms}}}$$

Integrator

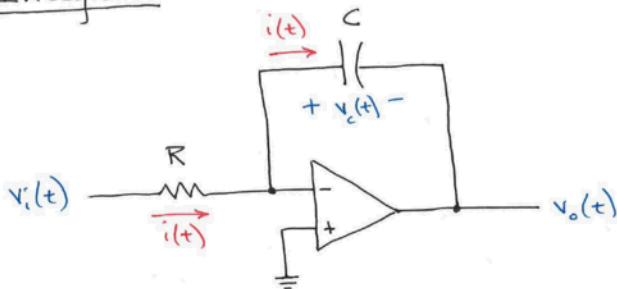

$$i(t) = \frac{v_i(t)}{R}$$

$$v_o(t) = -v_c(t) = - \left\{ v_c(0) + \frac{1}{C} \int_0^t i(\tau) d\tau \right\}$$

$$= -v_c(0) - \frac{1}{C} \int_0^t \frac{v_i(\tau)}{R} d\tau$$

$$= -v_c(0) - \frac{1}{RC} \int_0^t v_i(\tau) d\tau$$