

Chapter 7


Response of First-Order *RL* and *RC* Circuits

Learning Goals for Chapter 7

- Be able to calculate the complete response for first-order RL and RC circuits with constant inputs


Complete Response of RC and RL Circuits

- Voltages and currents in circuits that contain capacitors and inductors are solutions to differential equations.
- The order of the differential equation is usually equal to the total number of capacitors and inductors in the circuit.
- Circuits that contain only one capacitor or inductor can be represented by a first-order differential equation and are called first-order circuits.
- All first-order circuits are equivalent to one of the following:

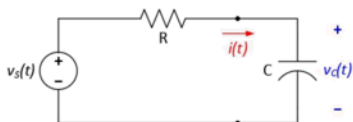

$$v_C(t) + RC \frac{dv_C(t)}{dt} = v_S(t)$$
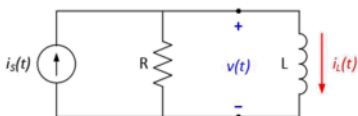
$$\frac{dv_C(t)}{dt} + \frac{v_C(t)}{RC} = \frac{v_S(t)}{RC}$$



$$i_L(t) + \frac{L}{R} \frac{di_L(t)}{dt} = i_S(t)$$

$$\frac{di_L(t)}{dt} + \frac{R}{L} i_L(t) = \frac{R}{L} i_S(t)$$

- These first-order differential equations have the same form:

$$\frac{dx(t)}{dt} + \frac{x(t)}{\tau} = \frac{y(t)}{\tau}$$

RC Circuit

$$y(t) = v_S(t)$$

$$x(t) = v_C(t)$$

$$\tau = RC$$

RL Circuit

$$y(t) = i_S(t)$$

$$x(t) = i_L(t)$$

$$\tau = \frac{L}{R}$$

- The constant τ is called the time constant.

- The solution to this first-order differential equation can be expressed in several equivalent forms:

complete response = transient response + steady-state response

complete response = natural response + forced response

complete response = homogeneous response + particular solution

- We will only consider first-order circuits with constant inputs.
- Solution approach:
 - Determine the initial condition of the energy storage element.
 - Determine the steady-state or forced response.
 - Add the natural response to the forced response to obtain the complete response. Use the initial condition to resolve the constant in the natural response.

Constant Input

$$y(t) = M = x(\infty)$$

Then:

$$\frac{dx(t)}{dt} + \frac{x(t)}{\tau} = \frac{M}{\tau}$$

$$\frac{dx(t)}{dt} = \frac{M - x(t)}{\tau}$$

$$\frac{dx(t)}{x(t) - M} = -\frac{dt}{\tau}$$

$$\int \frac{dx}{x - M} = -\frac{1}{\tau} \int dt$$

$$\ln(x - M) = -\frac{t}{\tau} + D$$

$$e^{\ln(x-M)} = e^{\frac{-t}{\tau} + D}$$

$$x - M = K e^{\frac{-t}{\tau}} \quad \text{where} \quad K = e^D$$

So the complete response is:

$$x(t) = M + K e^{\frac{-t}{\tau}}$$

At time $t = 0$:


$$x(0) = M + K$$

$$K = x(0) - M = x(0) - x(\infty)$$

Finally:


$$x(t) = x(\infty) + [x(0) - x(\infty)] e^{\frac{-t}{\tau}}$$

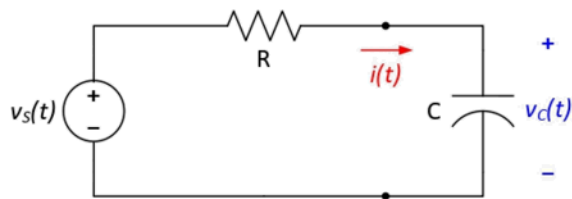- For the original RC circuit with $v_s(t) = M = x(\infty) = V_{OC}$:



$$v_C(t) = V_{OC} + [v_C(0) - V_{OC}]e^{\frac{-t}{RC}}$$

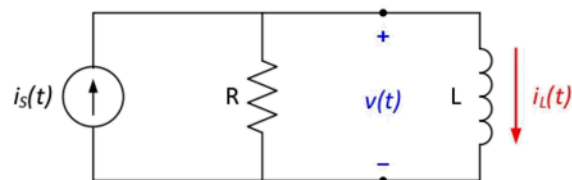- For the original RL circuit with $i_s(t) = M = x(\infty) = I_{SC}$:



$$i_L(t) = I_{SC} + [i_L(0) - I_{SC}]e^{\frac{-R}{L}t}$$

- These results can be shifted to time $t = t_0$:

$$v_C(t) = V_{OC} + [v_C(t_0) - V_{OC}]e^{\frac{-(t-t_0)}{RC}} \quad \text{for } t > t_0$$



$$i_L(t) = I_{SC} + [i_L(t_0) - I_{SC}]e^{\frac{-R}{L}(t-t_0)} \quad \text{for } t > t_0$$

First-order Circuits


- Circuits that contain only one energy storage element (a capacitor or an inductor) and resistors.
- Circuits may be energized by voltage sources and/or current sources.
- We will consider only circuits with constant (DC) voltage or current sources.

First-order Circuits

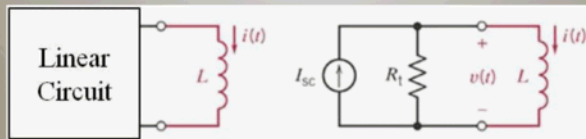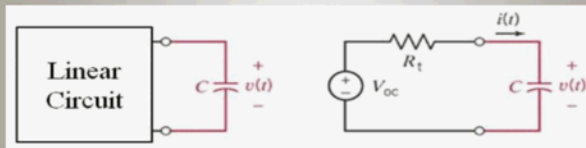- Any first-order circuit can be reduced to either a Thévenin equivalent or a Norton equivalent circuit of the following forms:



First-order Circuits

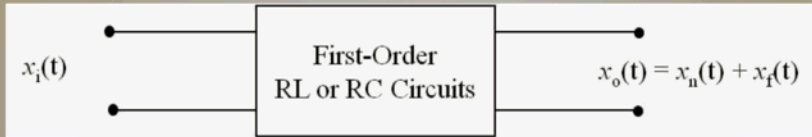

$$x_0(t) = x_n(t) + x_f(t)$$

- $x_0(t)$: complete response
- $x_n(t)$: natural, transient or homogeneous response
- $x_f(t)$: forced, steady-state or particular response


Complete Response to a Constant Input

- The complete response of the circuit is

$$x(t) = x(\infty) + [x(0) - x(\infty)]e^{-t/\tau}$$

- For a RC circuit (*find Thévenin Equivalent Circuit*)
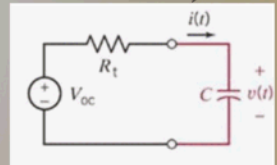
$$v_C(t) = v_{oc} + [v_C(0) - v_{oc}]e^{-t/\tau} \quad \text{where} \quad \tau = R_{th}C$$



- For a RL circuit (*find Norton Equivalent Circuit*),

$$i_L(t) = i_{sc} + [i_L(0) - i_{sc}]e^{-t/\tau} \quad \text{where} \quad \tau = \frac{L}{R_{th}}$$

