
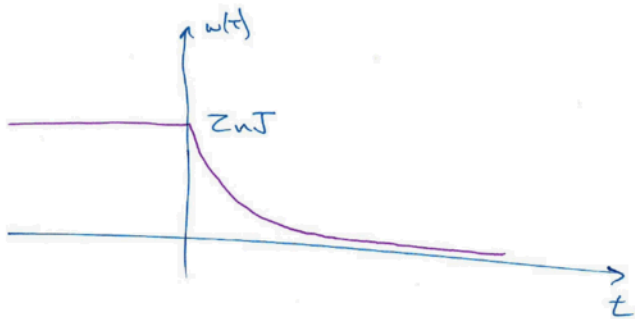


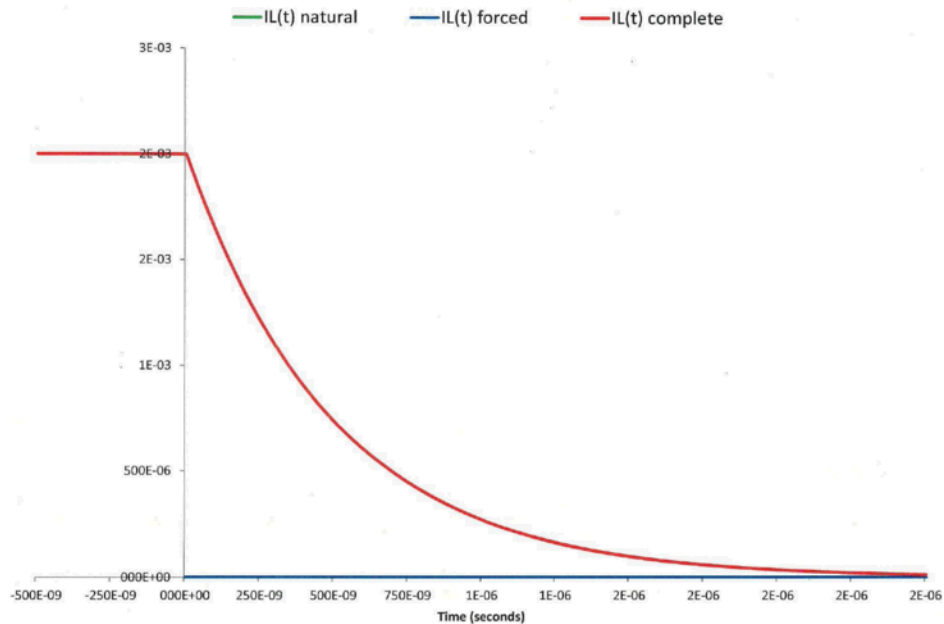
$$\begin{aligned}
 w(t) &= \frac{1}{2} L i_L^2(t) \\
 &= \frac{.001}{2} (.002 e^{-2 \times 10^6 t})^2 \\
 &= 2 \times 10^{-9} e^{-4 \times 10^6 t} \text{ J}
 \end{aligned}$$



Constant Source Response




Constant Source Response

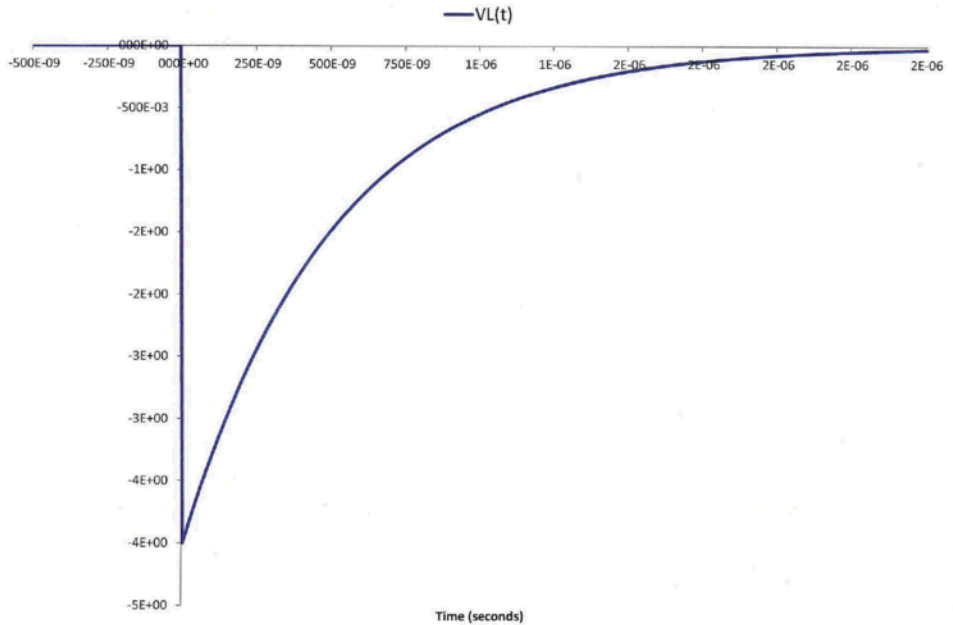


Constant Source Response

— PL(t) abs

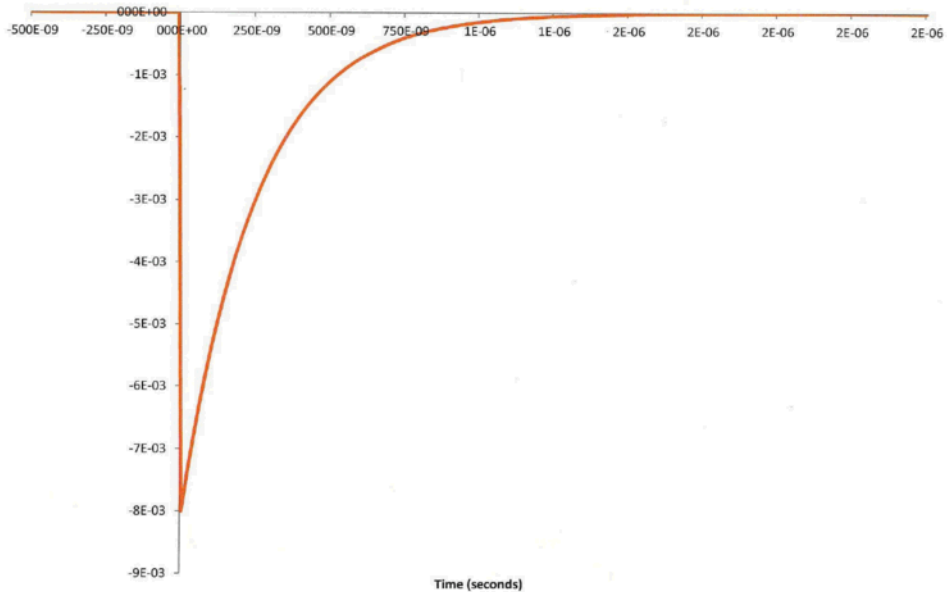


Constant Source Response

— WL(t)

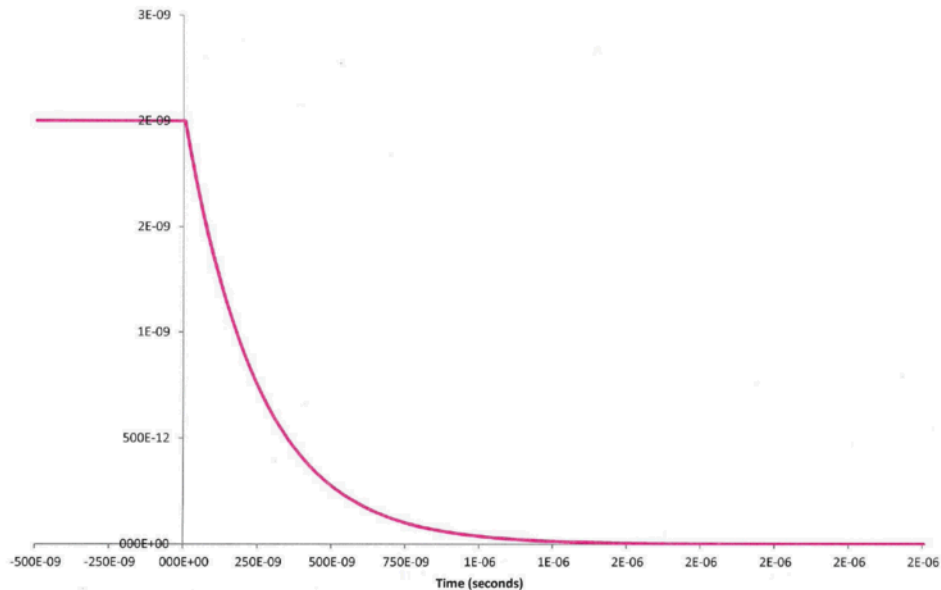


Example

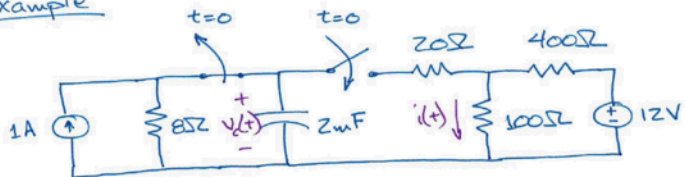


Determine $i(t)$.

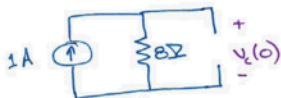- Determine the initial condition for the capacitor voltage $v_c(0)$.




$$v_c(0) = 1A(8\Omega) = 8V$$

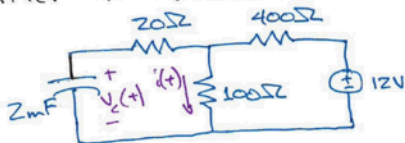- After the switches are thrown the circuit is:




$$v_c(0) = 8V$$

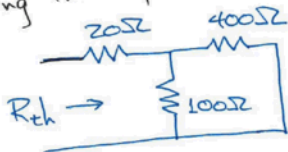- Find the Thevenin equivalent of the circuit facing the capacitor.



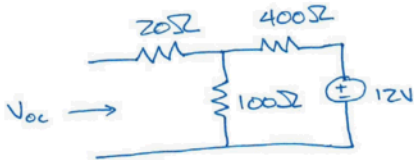
$$\begin{aligned} R_{th} &= 20 + 100 \parallel 400 \\ &= 20 + 80 \\ &= 100\Omega \end{aligned}$$



$$V_{oc} = \frac{100}{100+400} (12V) = 2.4V$$


- So our circuit is:

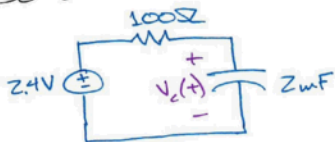

$$\begin{aligned} V_{oc} &= 2.4V \\ R &= 100\Omega \\ C &= 2mF \\ \tau &= RC = 0.2 \text{ sec} \\ v_c(0) &= 8V \end{aligned}$$

$$\begin{aligned} v_c(t) &= V_{oc} + [v_c(0) - V_{oc}] e^{-t/\tau} \\ &= 2.4 + (8 - 2.4) e^{-t/0.2} \\ &= 2.4 + 5.6 e^{-5t} \text{ V} \end{aligned}$$

- Now to find $i(t)$

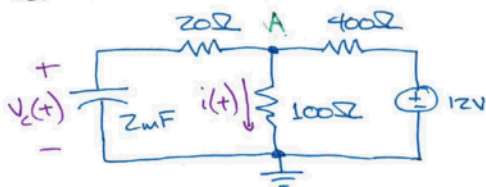

Write a KCL equation at Node A:

$$\frac{v_c(t) - v_a(t)}{20} + \frac{12 - v_a(t)}{400} = \frac{v_a(t)}{100}$$

$$20 \{ v_c(t) - v_a(t) \} + 12 - v_a(t) = 4v_a(t)$$

$$20v_c(t) - 20v_a(t) + 12 - v_a(t) = 4v_a(t)$$

$$v_a(t) = \frac{20v_c(t) + 12}{25}$$

$$i(t) = \frac{v_a(t)}{100}$$

$$= \frac{20v_c(t) + 12}{25 \cdot 100}$$


$$= .008v_c(t) + .0048$$

$$= .008 \{ 2.4 + 5.6e^{-5t} \} + .0048$$

$$= .024 + .0448e^{-5t} \text{ A}$$

$$= \underline{\underline{24 + 44.8e^{-5t} \text{ mA}}}$$


Constant Source Response

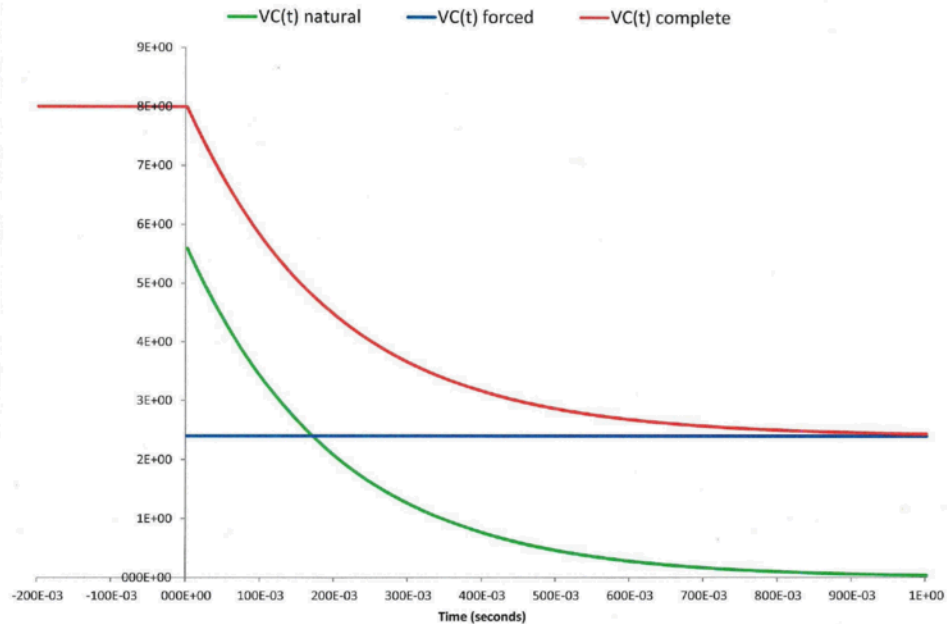

Unit Step Function


- Unit Step Function
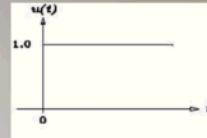
$$u(t) = \begin{cases} 0 & \text{for } t < 0 \\ 1 & \text{for } t \geq 0 \end{cases}$$




- Step Voltage Source
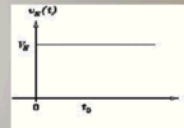
$$v_S(t) = V_S u(t) = \begin{cases} 0 & \text{for } t < 0 \\ V_S & \text{for } t \geq 0 \end{cases}$$



- Unit Step Function for $t_0 \neq 0$
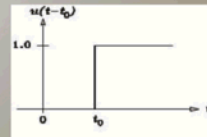
$$u(t - t_0) = \begin{cases} 0 & \text{for } t < t_0 \\ 1 & \text{for } t \geq t_0 \end{cases}$$



- Step Voltage Source for $t_0 \neq 0$

$$v_S(t) = V_S u(t - t_0) = \begin{cases} 0 & \text{for } t < t_0 \\ V_S & \text{for } t \geq t_0 \end{cases}$$

