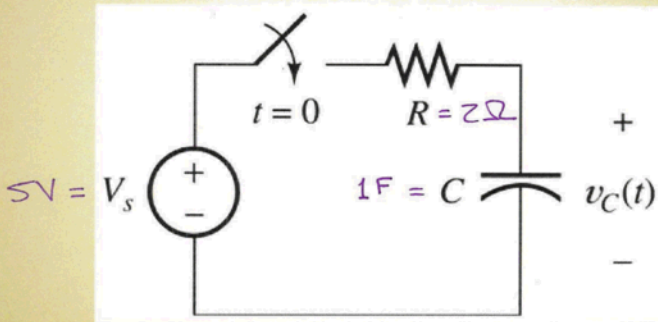



## Example 8.7.2 – RC Circuit

- Find the expression for the voltage across the capacitor when  $v_C(0^-) = 0$ .




$$\tau = RC$$

# Capacitor

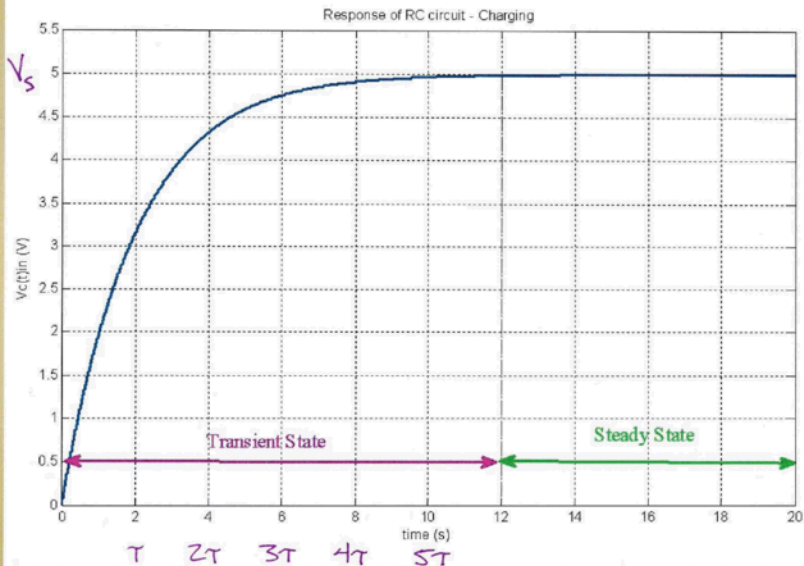

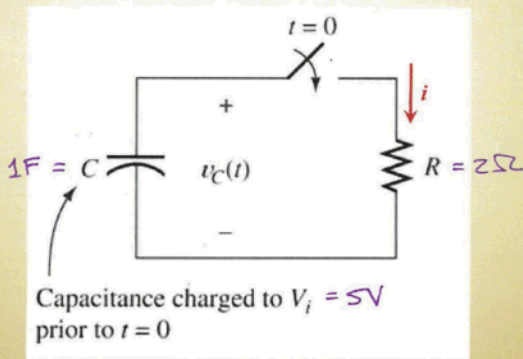
## Example 8.7.1 – Discharge of a Capacitance through a Resistance

- Find the natural response of the voltage across the capacitor when the switch is closed at  $t = 0$ . Initially, the capacitor is charged to a voltage  $V_i$



$$\tau = RC$$

# Capacitor

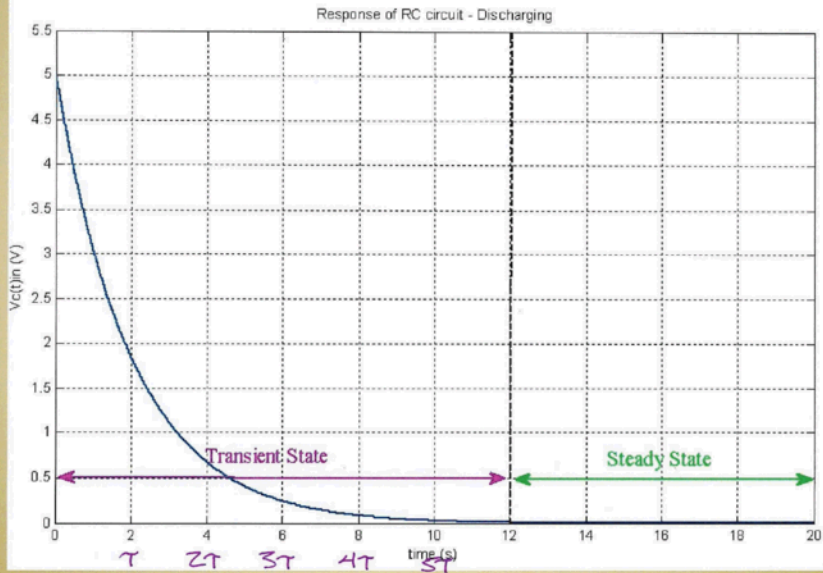

### Example 1a

$$v_c(t) = V_{oc} + [v_c(0) - V_{oc}] e^{-\frac{t}{RC}}$$

$$V_{oc} = V_s = 5V$$

$$R = 2\Omega$$

$$C = 1F$$

$$v_c(0) = 0$$

$$v_c(t) = 5 + [0 - 5] e^{-\frac{t}{2}} = 5 - 5e^{-\frac{t}{2}} V$$

### Example 1b

$$v_c(t) = V_{oc} + [v_c(0) - V_{oc}] e^{-\frac{t}{RC}}$$

$$V_{oc} = 0$$

$$R = 2\Omega$$


$$C = 1F$$

$$v_c(0) = 5V$$

$$v_c(t) = 0 + [5 - 0] e^{-\frac{t}{2}} = 5e^{-\frac{t}{2}} V$$

## Example 8.7.3 – RL Circuit


- Find the express of the current.

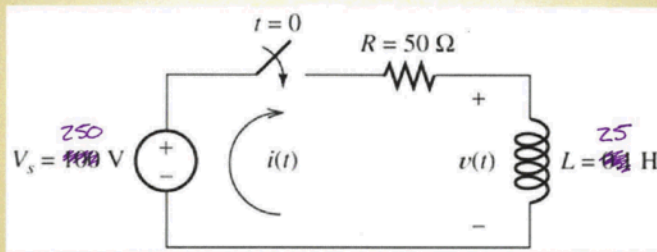


$$\tau = \frac{L}{R}$$



# Inductor

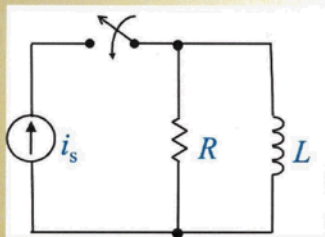


$$\tau = \frac{L}{R}$$

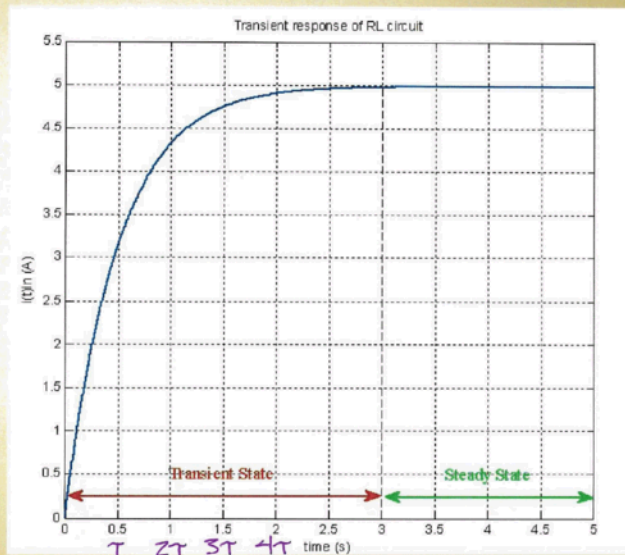

## Example 8.7.4 – RL Circuit


- Find the express of the current

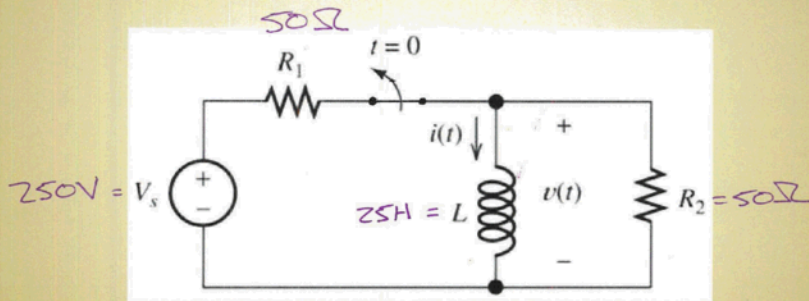


$$\tau = \frac{L}{R}$$



# Inductor

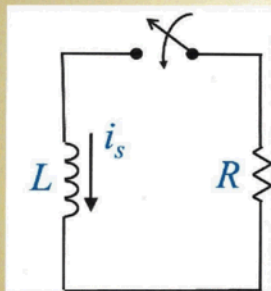

$$\tau = \frac{L}{R}$$

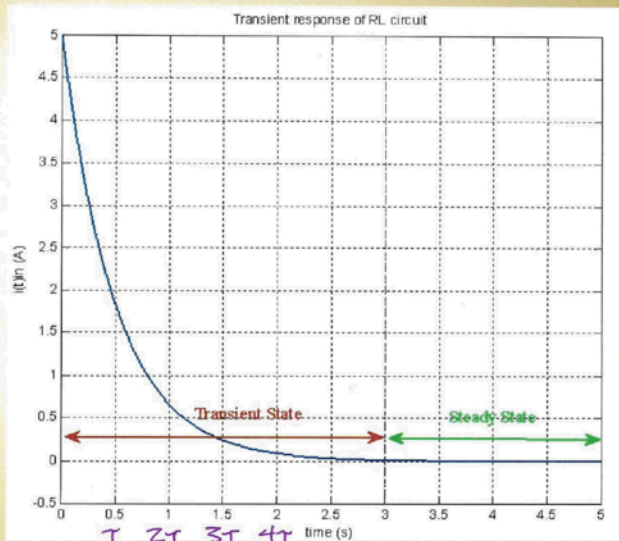

### Example 2a

$$i_L(t) = I_{sc} + [i_L(0) - I_{sc}] e^{-\frac{R}{L}t}$$

$$I_{sc} = \frac{250}{50} = 5A$$

$$R = 50\Omega$$

$$L = 25H$$

$$i_L(0) = 0$$

$$i_L(t) = 5 + [0 - 5] e^{-2t} = 5 - 5e^{-2t} A$$

### Example 2b

$$i_L(t) = I_{sc} + [i_L(0) - I_{sc}] e^{-\frac{R}{L}t}$$

$$I_{sc} = 0$$

$$R = 50\Omega$$

$$L = 25H$$

$$i_L(0) = \frac{250}{50} = 5A$$

$$i_L(t) = 0 + [5 - 0] e^{-2t} = 5e^{-2t} A$$