

$$e^{-1} = 0.3679$$

$$1 - e^{-1} = 0.6321$$

$$e^{-2} = 0.1353$$

$$1 - e^{-2} = 0.8647$$

$$e^{-3} = 0.0498$$

$$1 - e^{-3} = 0.9502$$

$$e^{-4} = 0.0183$$


$$1 - e^{-4} = 0.9817$$


$$e^{-5} = 0.0067$$

$$1 - e^{-5} = 0.9933$$

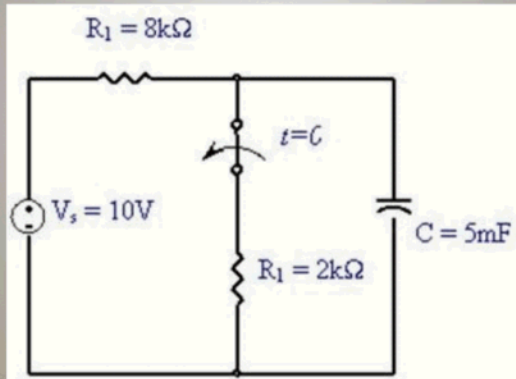Example 8.7.5 – RC Circuit


- Find the voltage across the capacitor when the switch is open at $t = 0$.



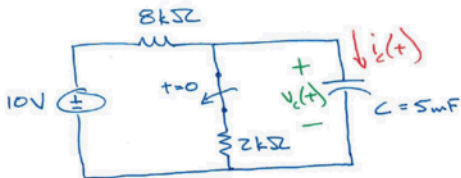

- Determine the initial condition.

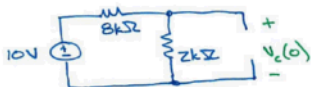Prior to $t=0$ the circuit is assumed to be in the steady state so $i_c = C \frac{dv_c(t)}{dt} = 0$.



$$v_c(0) = \frac{2k\Omega}{8k\Omega + 2k\Omega} (10V) = 2V$$


- After the switch is opened the steady state will be:




$$V_{oc} = 10V = v_c(\infty)$$

$$\tau = RC = 40 \text{ sec}$$

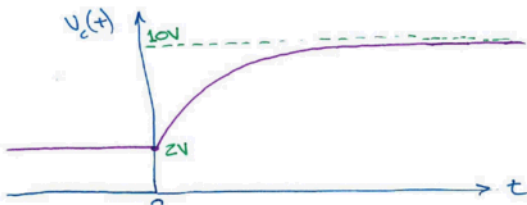
$$\begin{aligned} v_c(t) &= V_{oc} + \{v_c(0) - V_{oc}\} e^{-\frac{t}{\tau}} \\ &= 10 + (2 - 10)e^{-\frac{t}{40}} = 10 - 8e^{-\frac{t}{40}} \text{ V} \end{aligned}$$



Constant Source Response

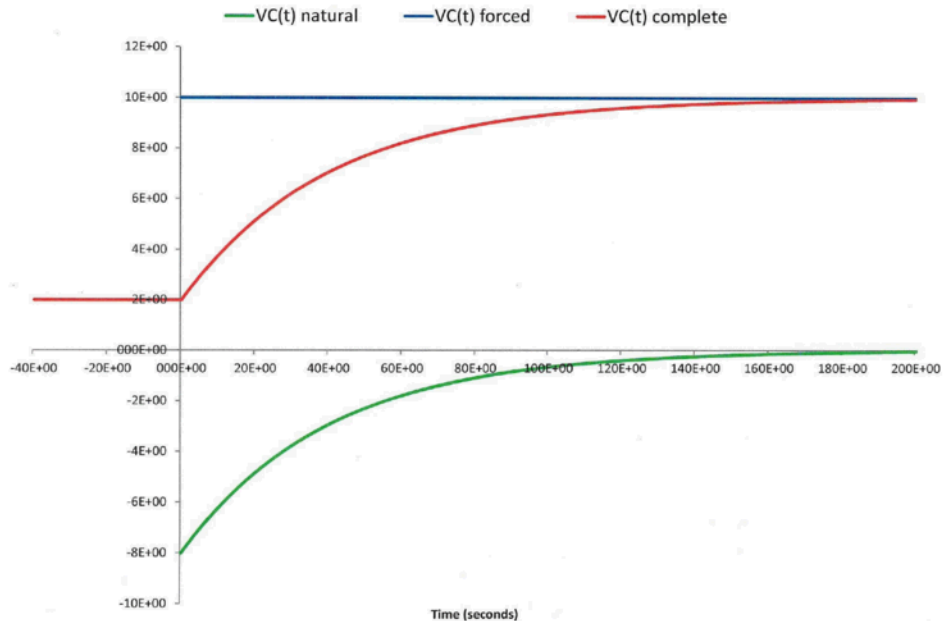


Constant Source Response

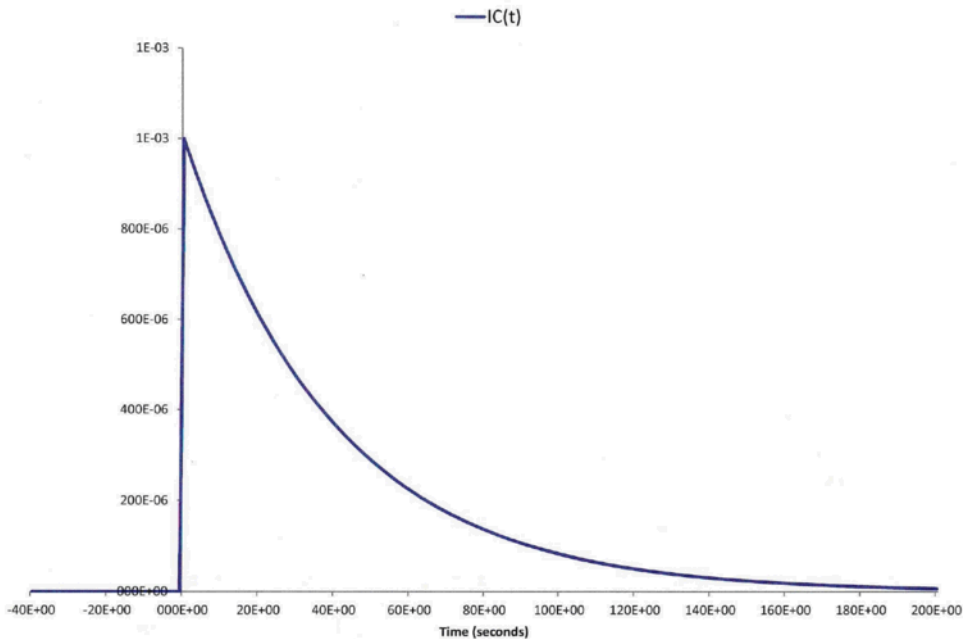


Constant Source Response

— PC(t) abs

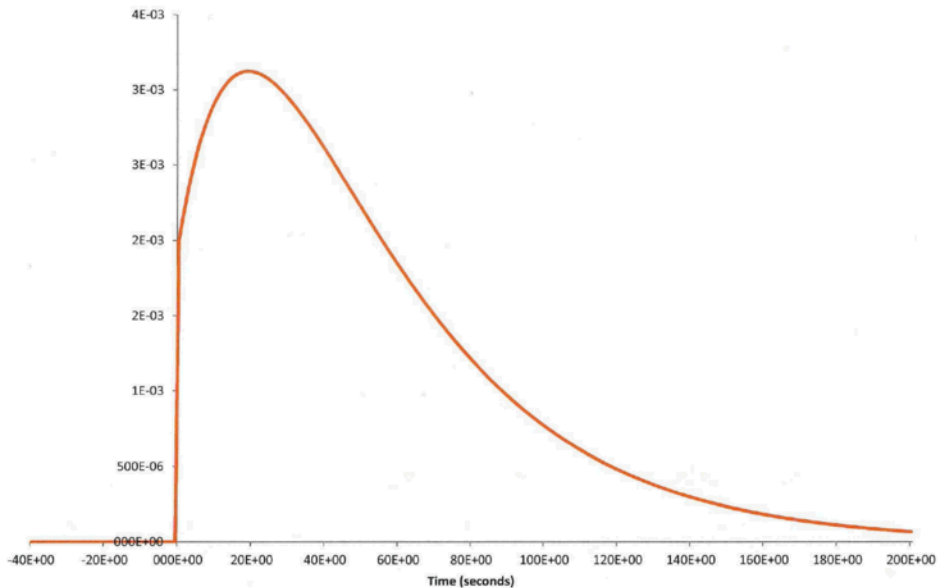


Constant Source Response


WC(t)

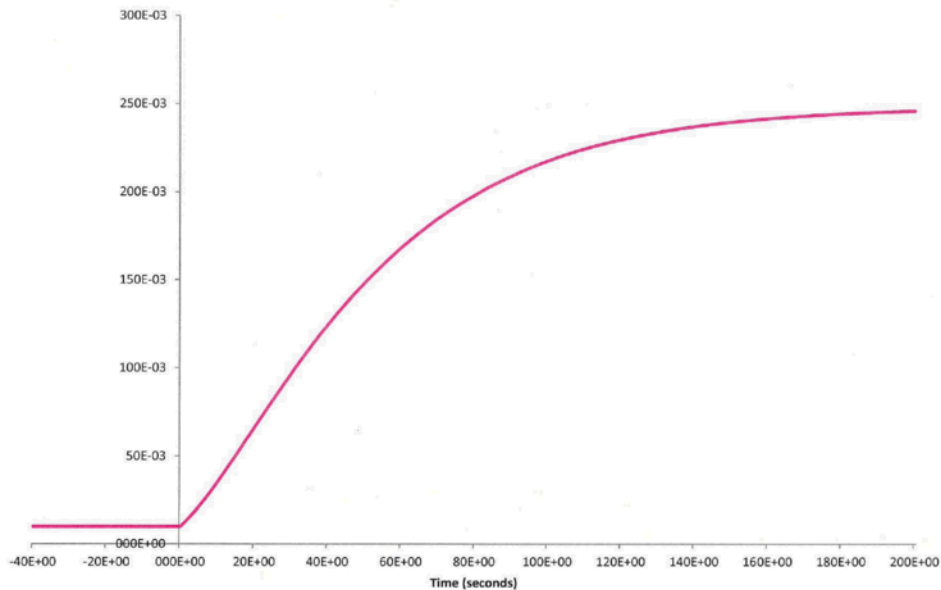

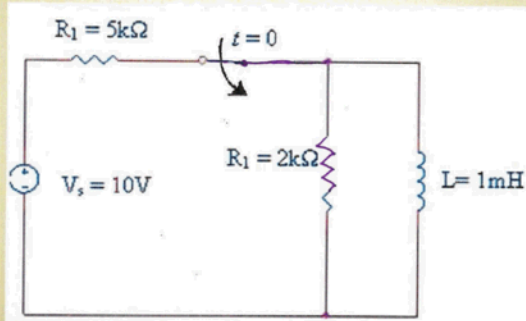
Example 8.7.6 – *RL* Circuit

- Find the expression for the current going through the inductor after the switch is open



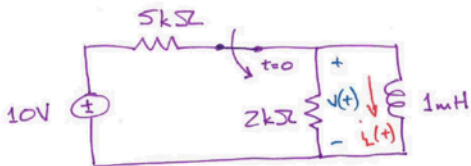

Determine the initial inductor current.

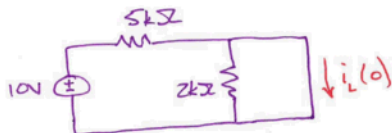

$$i_L(0) = \frac{10V}{5k\Omega} = 2mA$$

After the switch is opened



$$I_{sc} = 0$$

$$R = 2k\Omega$$

$$L = 1mH$$



$$i_L(0) = 2mA$$

$$i_L(t) = I_{sc} + [i_L(0) - I_{sc}] e^{-\frac{R}{L}t}$$

$$= 0 + [0.002 - 0] e^{-\frac{2000}{.001}t}$$

$$= .002 e^{-2 \times 10^6 t} \text{ A}$$
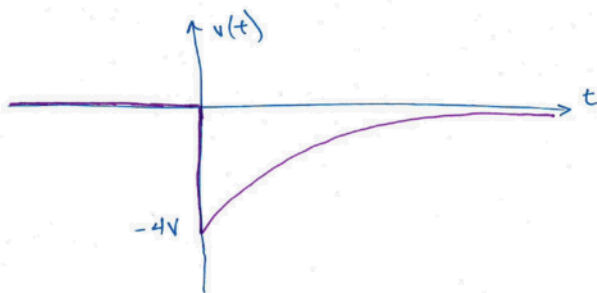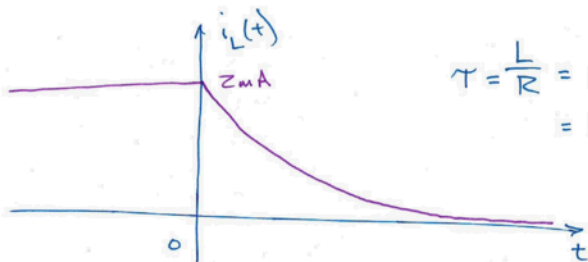
$$V(t) = L \frac{di_L(t)}{dt} = (.001)(.002)(-2 \times 10^6 e^{-2 \times 10^6 t}) = -4eV$$



$$P_{\text{abs}}(t) = i_L(t)v(t) = -.008 e^{-4 \times 10^6 t} \text{ W}$$

$$P_{\text{sup}}(t) = -P_{\text{abs}}(t) = .008 e^{-4 \times 10^6 t} \text{ W}$$

