
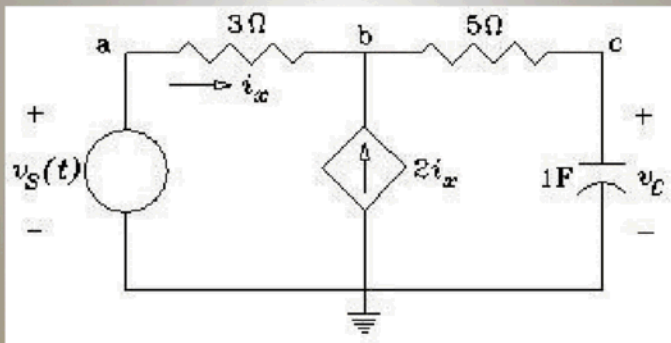


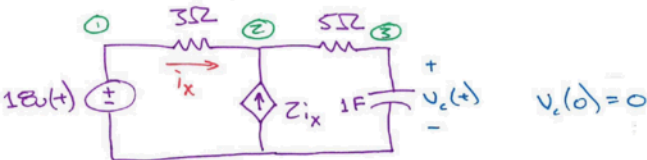Example 8.7.14 – RC Circuit with Dependent Source


- Consider the circuit shown with a controlled current source. The circuit is initially at rest. Find the complete response of the capacitor voltage. The source voltage is $v_S(t) = 18 u(t)$.





Find $V_c(t)$

• Determine a Thevenin equivalent.

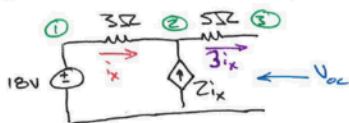

KCL at Node 2:


$$i_x + Z i_x = 3 i_x$$

Because of the open circuit:

$$3 i_x = 0$$

$$i_x = 0$$

$$V_{oc} = 18V$$

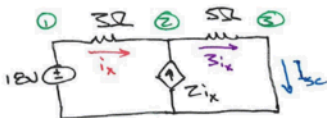

KCL at Node 2:

$$i_x + Z i_x = 3 i_x$$

KVL around outer loop:


$$-18 + 3 i_x + 5(3 i_x) = 0$$

$$18 i_x = 18$$

$$i_x = 1$$

$$I_{sc} = 3 i_x = 3A$$
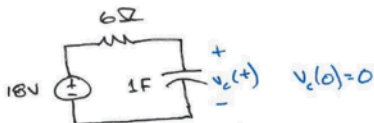
$$R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{18V}{3A} = 6\Omega$$



$$V_{oc} = 18V$$

$$R = 6\Omega$$


$$C = 1F$$

$$\tau = RC = 6 \text{ sec}$$

• So, $V_c(t) = V_{oc} + [V_c(0) - V_{\infty}] e^{-t/\tau}$


$$= 18 - 18 e^{-t/6} V$$

Constant Source Response

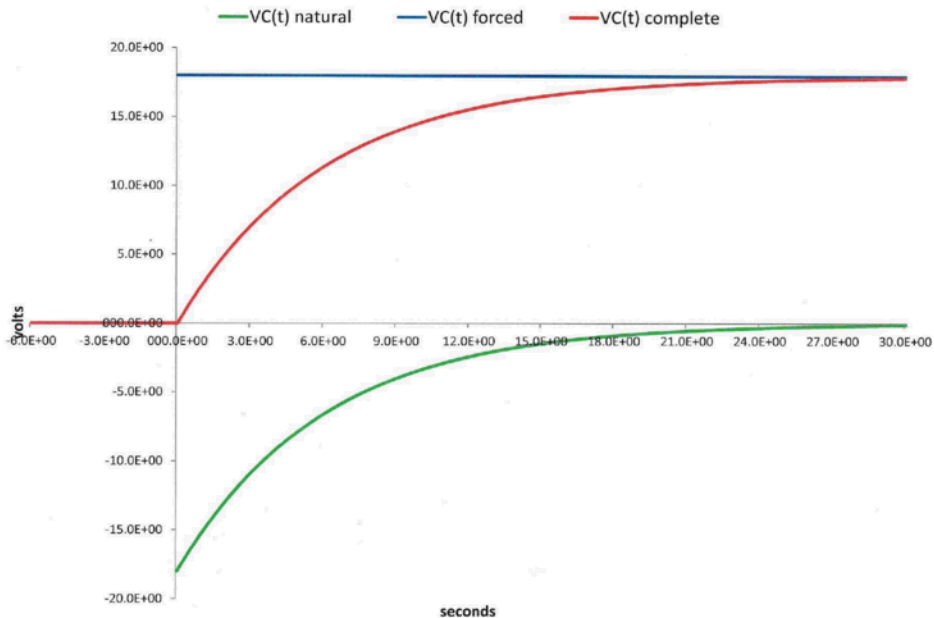


RL Example

Determine $i_L(t)$ and $v_L(t)$.

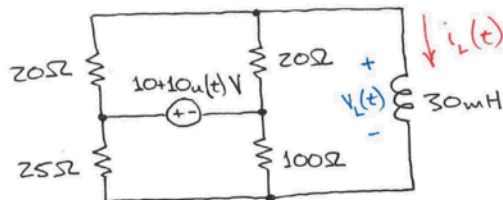

First find $i_L(0)$.

In the steady-state just prior to $t=0$:

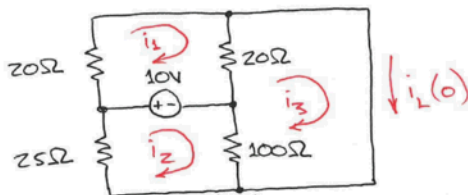

Mesh current equations:

$$20i_1 + 20(i_1 - i_3) - 10 = 0$$


$$25i_2 + 10 + 100(i_2 - i_3) = 0$$

$$20(i_3 - i_1) + 100(i_3 - i_2) = 0$$

$$\begin{bmatrix} 40 & 0 & -20 \\ 0 & 125 & -100 \\ -20 & -100 & 120 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 10 \\ -10 \\ 0 \end{bmatrix}$$

From which $i_3 = i_L(0) = -0.1 \text{ A}$

Or using node voltage equations:

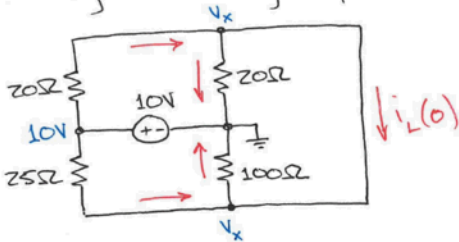

$$\frac{10 - V_x}{20} = i_L(0) + \frac{V_x}{20}$$

$$\frac{10 - V_x}{25} + i_L(0) = \frac{V_x}{100}$$

$$\frac{10 - V_x}{20} - \frac{V_x}{20} = i_L(0)$$

$$\frac{10 - V_x}{25} - \frac{V_x}{100} = -i_L(0)$$



$$\frac{10 - V_x}{20} - \frac{V_x}{20} + \frac{10 - V_x}{25} - \frac{V_x}{100} = 0$$

From which:


$$V_x = 6V$$

$$i_L(0) = \frac{10 - 6}{20} - \frac{6}{20} = -0.1A \text{ (as before)}$$

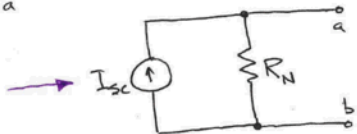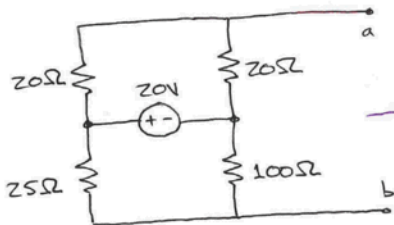Next find the Norton equivalent for $t \geq 0$




For I_{sc} :

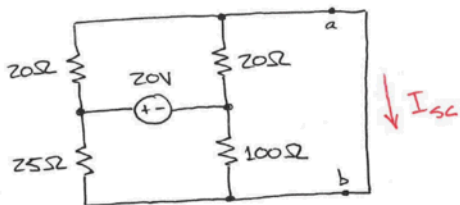

This is the same circuit as the one for finding $i_L(0)$ except the voltage source is doubled (20V vs. 10V).
Therefore:


$$I_{sc} = 2 i_L(0) = -0.2A$$

For R_N :

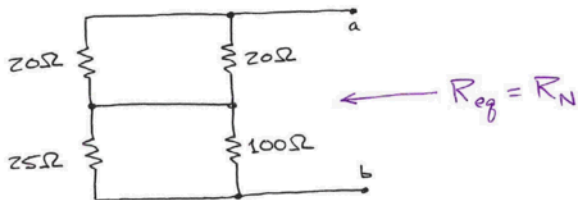

$$\begin{aligned} R_{eq} &= 20\Omega \parallel 20\Omega + 25\Omega \parallel 100\Omega \\ &= 10\Omega + 20\Omega \\ &= 30\Omega \end{aligned}$$

S0,

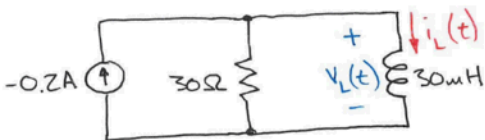

$$i_L(0) = -0.1 \text{ A}$$

$$I_{sc} = -0.2 \text{ A}$$

$$\tau = \frac{L}{R_N} = \frac{.03}{30} = 1 \text{ ms}$$


$$\begin{aligned} i_L(t) &= I_{sc} + [i_L(0) - I_{sc}] e^{-t/\tau} \\ &= -0.2 + [-0.1 - (-0.2)] e^{-t/.001} \\ &= \underline{\underline{-0.2 + 0.1 e^{-1000t} \text{ A}}} \end{aligned}$$

$$v_L(t) = L \frac{di_L}{dt}$$


$$= 0.03 (0.1) (-1000) e^{-1000t}$$

$$= \underline{\underline{-3 e^{-1000t} \text{ V}}}$$


L: Current

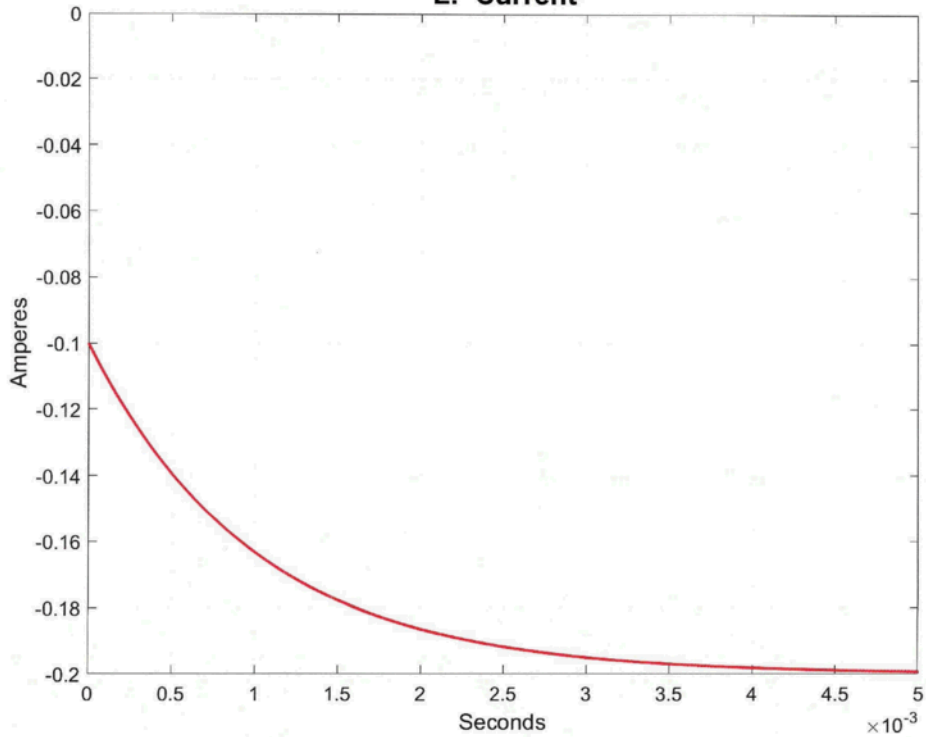

L: Voltage

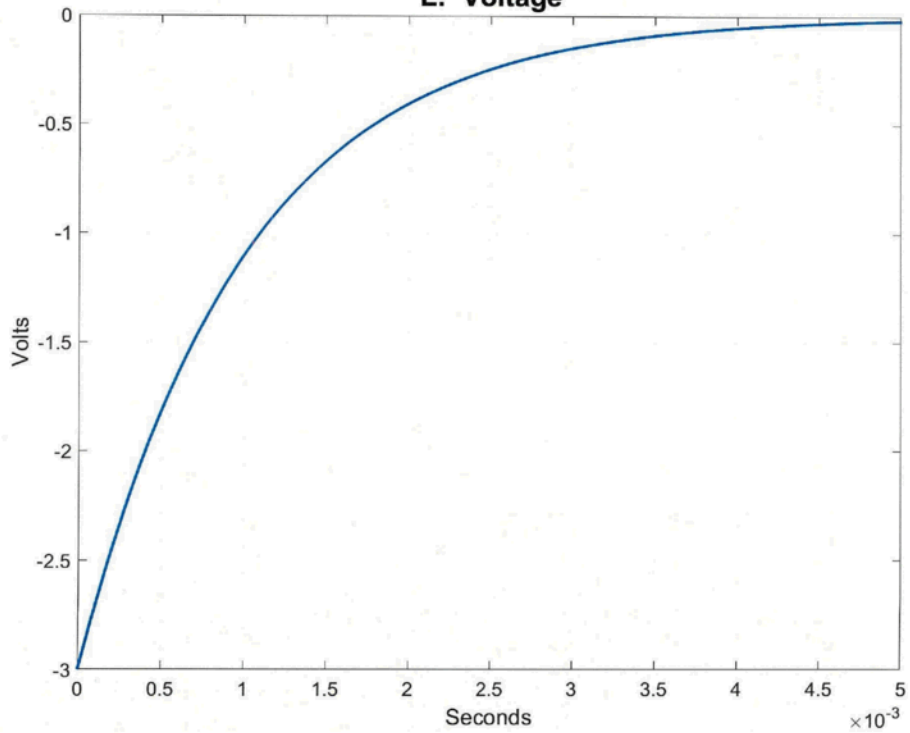


Example

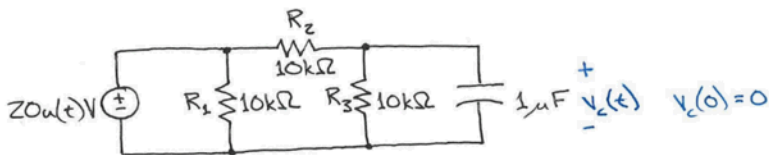

- Determine the capacitor voltage, current, power absorbed and stored energy.
- Determine the power absorbed by the resistors.
- Determine the power supplied by the source.
- Evaluate these expressions for $t = 10\text{ ms}$.

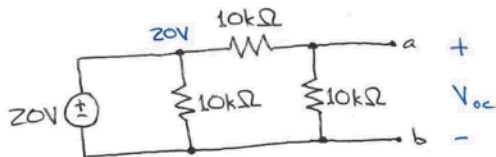First find the Thevenin equivalent circuit facing the capacitor for $t \geq 0$:



By voltage division:

$$V_{oc} = \frac{10}{10+10} (20) = 10V$$