
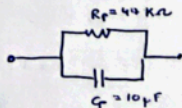


**P8** → T.4

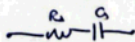no es posible ya que  $\omega \approx 30 \text{ Hz}$



$\Leftrightarrow$



a)  $f = 1000 \text{ Hz}$

b)  $f = 10000 \text{ Hz}$

$$Z_{\text{parallel}} = R_P \parallel \frac{1}{j\omega C_P} \rightarrow \frac{1}{Z_P} = \frac{1}{R_P} + j\omega C_P \rightarrow Z_P = \frac{R_P}{1 + j\omega R_P C_P}$$

↓ multiplicamos arriba y abajo por  $(1 - j\omega R_P C_P)$

$$Z_P = \frac{R_P - j\omega R_P^2 C_P}{1 + \omega^2 R_P^2 C_P^2}$$

$$Z_{\text{serie}} = R_s + \frac{1}{j\omega C_s} = R_s - j/\omega C_s$$

$$\begin{aligned} \text{a) } \rightarrow Z_P &= \frac{R_P}{1 + \omega^2 R_P^2 C_P^2} - \frac{j\omega R_P^2 C_P}{1 + \omega^2 R_P^2 C_P^2} \\ Z_s &= R_s - j/\omega C_s \end{aligned} \quad \left. \vphantom{\begin{aligned} \text{a) } \rightarrow Z_P &= \frac{R_P}{1 + \omega^2 R_P^2 C_P^2} - \frac{j\omega R_P^2 C_P}{1 + \omega^2 R_P^2 C_P^2} \\ Z_s &= R_s - j/\omega C_s \end{aligned}} \right\} \rightarrow$$

Igualamos ambas impedancias, las reales con las reales y las imaginarias con las imaginarias

→ Dependiendo de la frecuencia

Real  $\rightarrow R_s = \frac{R_P}{1 + \omega^2 R_P^2 C_P^2}$  (1)


Im  $\rightarrow \frac{1}{\omega C_s} = \frac{\omega R_P^2 C_P}{1 + \omega^2 R_P^2 C_P^2}$  (2)

Substituyendo valores de  $R_P$  y  $C_P$  en las ecuaciones (1) y (2)

a)  $f = 1000 \text{ Hz}$   $\rightarrow \omega = 2\pi \cdot 10^3 \text{ s}^{-1} \rightarrow R_s = 4323 \Omega, C_s = 12415 \text{ nF}$

b)  $f = 10000 \text{ Hz}$   $\rightarrow \omega = 2\pi \cdot 10^4 \text{ s}^{-1} \rightarrow R_s = 49313 \Omega, C_s = 11115 \text{ nF}$

P9

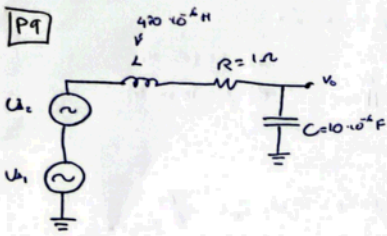


$$U_1(t) = 300 \sin(2\pi f t) \text{ V}$$

$$U_2(t) = 60 \sin(2\pi f t + 2\pi') \text{ V}$$

$$f = 1000 \text{ Hz}$$

$$\omega = 10000 \text{ rad/s}$$

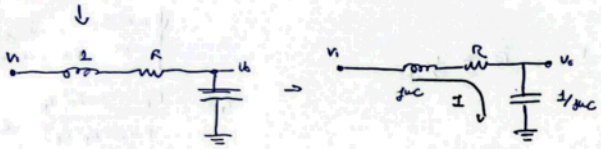


$$\frac{V_0}{V_1} = \frac{j\omega C}{\frac{1}{j\omega C} + j\omega L + R} = \frac{1}{1 - \omega^2 LC + j\omega RC} = T(\omega)$$

$$\vec{V}_0 = \vec{V}_1 \cdot T(\omega) \rightarrow T(\omega) = |T(\omega)| \angle \varphi_T = \frac{1}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}} \angle 0 - \varphi_T - \left( \frac{\omega RC}{1 - \omega^2 LC} \right)$$

from before  $T(\omega)$


~~Substituir valores T(ω)~~

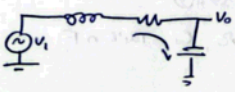Al dar i fides de posici3 aplicamos el principio de superposici3n:



$$U_1 = 300 \angle 0^\circ \rightarrow V_{01} = 300 \text{ V } \angle 0^\circ \times T(\omega) \rightarrow \text{Substituir}$$
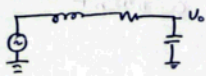
$$300 \text{ V } \angle 0^\circ \times 1.2242 \cdot 10^{-4} \angle -91.41^\circ = \boxed{36.726 \text{ V } \angle -91.41^\circ}$$




$$U_2 = 60 \angle 22^\circ \rightarrow V_{02} = 60 \angle 22^\circ \times T(\omega)$$

$$60 \angle 22^\circ \times (0.6549 \angle -93.95^\circ) = \boxed{39.294 \text{ V } \angle -71.95^\circ}$$

$V_0$  es la suma de ambas  $\rightarrow V_0(t) = 36.726 \sin(2\pi f t - 91.41^\circ) + 39.294 \sin(2\pi f t - 71.95^\circ)$

P10

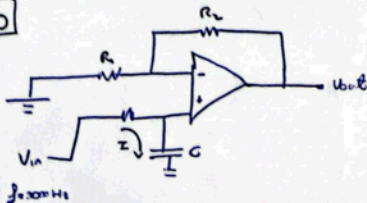

$$R = 5300 \Omega \quad | \quad R_1 = 10 \text{ K}\Omega$$

$$C = 10 \text{ nF} \quad | \quad R_2 = 27 \text{ K}\Omega$$

$$V_{in} = 1 \text{ V} \sin(2\pi \cdot 3000 \text{ Hz} \cdot t)$$

$$V^+ = V_{in} \frac{Z_C}{R + Z_C} = V_{in} \frac{1/j\omega C}{R + 1/j\omega C} = \frac{V_{in}}{1 + j\omega RC}$$

$$\frac{V_{out} \cdot R_2}{R_1} = \frac{V^+ - 0}{R_1} \Rightarrow V_{out} = V^+ \left(1 + \frac{R_2}{R_1}\right)$$

$$V^+ = V^- \Rightarrow V_{out} = \left(1 + \frac{R_2}{R_1}\right) \cdot \frac{1}{1 + j\omega RC} V_{in}$$


$$V_{in} = 1 \text{ V} \cdot 10^\circ$$

$$\left(1 + \frac{R_2}{R_1}\right) \frac{1}{1 + j\omega RC} = \left(1 + \frac{27}{10}\right) = \frac{1}{1 + j \underbrace{22 \cdot 3000 \cdot 5300 \cdot 10^{-9}}_{0.9999}} \text{ F}$$

$$= \frac{1 + 27/10}{\sqrt{1 + (0.9999)^2}} \angle 0 - \tan^{-1}(0.9999)$$


$$V_{out} = 2.6176 \text{ V} \angle -44.99^\circ$$
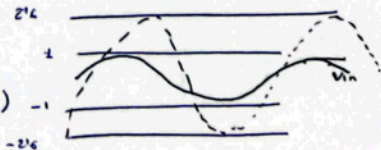
$$V_{out} = 2.6176 \text{ V} \cdot \sin(2\pi \cdot 3000 - 44.99^\circ)$$



$$\omega T = 300^\circ \rightarrow \frac{\omega}{2\pi} \cdot \frac{45}{360} \approx \frac{1}{8} \approx \text{delay} = \frac{1}{8}$$

P11

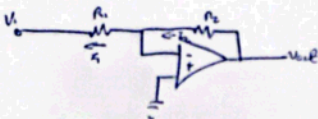

$$A_{d0} = 200\,000 \rightarrow 0\,dB \approx 200\,000$$

$$f_0 = 5\,Hz \rightarrow \text{lowpass}$$

$$A_d(f) = \frac{A_{d0}}{1 + j f/f_0}$$

General amplified  $V_o/V_i$  on  $f_{ac} \approx f$

$$R_1 = 220\,000\, \Omega \quad R_2 = 220\,000$$

$$I_1 = I_2 \rightarrow \frac{V^- - V_i}{R_1} = \frac{V_o - V^-}{R_2} \rightarrow \frac{R_2}{R_1} (V^- - V_i) = (V_o - V^-)$$

$$V_o = V^- \left(1 + \frac{R_2}{R_1}\right) - V_i \frac{R_2}{R_1}$$

$$V_o = A_d (V^+ - V^-) = -A_d V^- \rightarrow V^- = -V_o/A_d \rightarrow \text{on } V^- \text{ and } V_i$$

$\hookrightarrow V^+ = 0 \rightarrow \text{lowpass}$

$$V_o = -\frac{V_o}{A_d} \left(1 + \frac{R_2}{R_1}\right) - V_i \frac{R_2}{R_1} \rightarrow V_o \cdot \left[1 + \frac{1 + R_2/R_1}{A_d}\right] = -V_i \frac{R_2}{R_1}$$

$$\frac{V_o}{V_i} = \frac{-R_2/R_1}{1 + \frac{1 + R_2/R_1}{A_d}} \Rightarrow \frac{-R_2/R_1}{1 + \left(1 + \frac{R_2}{R_1}\right) \cdot \frac{1 + j f/f_0}{A_{d0}}} \quad \text{substit}$$

$$G = \frac{V_o}{V_i} = \frac{-220/512}{1 + \frac{1 + \frac{220}{512}}{200\,000} + j \frac{d \cdot C_1 + \frac{220}{512}}{200\,000 \cdot 5}}$$

P12

$$V_m = 5V$$

$$R = 412 \Omega$$

$$L = 22 \mu H$$

$$C = 100 nF$$

$$f_1 = 110 kHz$$


$$f_2 = 63 kHz$$

$$f_3 = 36 kHz$$

$$f_4 = 30 kHz$$

$$f_5 = 21 kHz$$

$$f_6 = 36 kHz$$

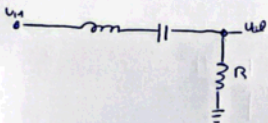

Señala que en el nodo anterior, las corrientes de flujo en:

$$V_n = \frac{4 V_m}{n \pi} \sin\left(\frac{n \pi t}{2}\right)$$

La función vectorial dada por la función de transferencia según la frecuencia como la impedancia en serie

$$Z(\omega) = R + j\left(\omega L - \frac{1}{\omega C}\right) \rightarrow |Z(\omega)| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$\text{Señala que } H(\omega) = \frac{V_n}{V_m} = \frac{1}{|Z(\omega)|} = \frac{1}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

Antes calcula las amplitudes para cada  $f$

$f$	$V_n$	$H(f)$	$V_{out}$
$f_1 = 110 kHz$	0.7662	0.2983	2.5958 ✓
$f_2 = 110 kHz$	0.1362	0.0047	4.26613 ✓
$f_3 = 3 \cdot 110 = 330 kHz$	0.12	0.01367	2.12271 ✓
$f_4 = 5 \cdot 110 = 550 kHz$	0.0732		

Si queremos usar

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$H = \frac{1}{\sqrt{1 + \left(\frac{f}{f_0} - \frac{f_0}{f}\right)^2}}$$

$$f_0 = 110 \text{ kHz}$$

	$V_n$	$H_2$	$V_{out} = \frac{V_n \cdot H_2}{f_n}$
$f_1 = 110 \text{ kHz}$	6'3662	0'2102	1'3332
$f_0 = 330 \text{ kHz}$	2'1221	0'02435	0'051673 V $\rightarrow$
$f_2 = 550 \text{ kHz}$	1'2732	0'01365	0'017329 $\rightarrow$ V

$f_1 = 63 \text{ Hz}$	6'3662	0'03811	0'3699 V
$f_3 = 199 \text{ Hz}$	2'1221	0'05492	0'11655 V
$f_5 = 315 \text{ Hz}$	1'2732	0'025789	0'03285 V



P13

$$f_0 = 12 \text{ kHz}, Q = 10, H_0 = 5, u_0 = 0.6 \text{ V}, f = 4 \text{ MHz}$$

$$V_3(t) = \frac{4 \cdot V_3}{\pi} \left( \sin(\omega_1 t) + \frac{\sin(\omega_1 t \cdot 3)}{3} + \frac{\sin(\omega_1 t \cdot 5)}{5} + \dots \right)$$

$$V_3 = \frac{4 \cdot 0.6}{\pi} \cdot \sin(2\pi \cdot 4000 t + \phi) + \frac{\sin(2\pi \cdot 3 \cdot 4000 t + \phi)}{3}$$

$$H(\omega) = \frac{H_0 \cdot \frac{\omega}{Q \omega_0}}{1 - \left(\frac{\omega}{\omega_0}\right)^2 + j \frac{\omega}{Q \omega_0}} \rightarrow |H(\omega)| = \frac{H_0 \cdot \frac{\omega}{Q \omega_0}}{\sqrt{\left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right)^2 + \left(\frac{\omega}{Q \omega_0}\right)^2}}$$

$$V_{0n} = u_n |H(\omega)|$$

$$\text{Calcul } H(4000) = \frac{5 \cdot \frac{2\pi \cdot 4000}{10 \cdot 2\pi \cdot 12000}}{\sqrt{\left(1 - \left(\frac{2\pi \cdot 4000}{2\pi \cdot 12000}\right)^2\right)^2 + \left(\frac{2\pi \cdot 4000}{10 \cdot 2\pi \cdot 12000}\right)^2}} = 1.0737$$

$$|H(12000)| = 50$$

$$\text{Calcul } V_{3n} \rightarrow V_{2n} = \frac{4 \cdot V_3}{\pi n} \cdot \sin\left(\frac{n\pi}{2}\right) =$$

$$V_{31} = \frac{4 \cdot 0.6}{\pi} = 1.019$$

$$V_{33} = \frac{4 \cdot 0.6}{3\pi} \cdot \sin\left(\frac{3\pi}{2}\right) = 16.1977$$


$$V_{0T} = V_{01} + V_{03} = 13.885 \text{ V}$$

Define  $\phi = \arctan \frac{\text{Im}[H(\omega)]}{\text{Re}[H(\omega)]} = \frac{5 \cdot \frac{4}{12} \sqrt{10^4 + 10^2}}{118732} = 87.85^\circ$

$$V_3 = 118732 \cdot \sin(22.4000 \cdot t + 87.85) + 161922 \sin(222.12000 \cdot t + 0^\circ)$$



P14

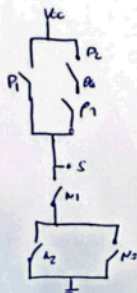

$$\begin{aligned}
 P & \quad w_1, p_1 \text{ cable } = E_1 \\
 & \quad w_2, p_2 \text{ cable } = E_2 \\
 & \quad w_3, p_3 \text{ cable } = E_3
 \end{aligned}$$

olena y segunda funci

$$\begin{aligned}
 S, \quad S=0 & \rightarrow \text{biene} \\
 \text{f} \quad S=1 & \rightarrow V_{cc}
 \end{aligned}$$

$$R_c \quad S=0 \rightarrow w_1 \text{ cable } y \quad w_2 = w_3 \text{ cable } = \text{cable}$$

$$w_1 \text{ AND } (w_2 = w_3)$$

Al otro cable para  $E_1$

$$E_1 \text{ AND } (E_2 \text{ OR } E_3)$$

$E_1$	$E_2$	$E_3$	$E_2 \text{ OR } E_3$	$E_1 \text{ AND } (E_2 \text{ OR } E_3)$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	1	0
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

8. Para  $Q_{10}$  or

$E_2$	$E_3$	$E_2 \text{ or } E_3$
0	0	0
0	1	1
1	0	1
1	1	1

porque si es 1

Por:  $S=1 \rightarrow$  la salida lógica sea la misma de la función para  $S=0$

$$E_1 \wedge (E_2 \vee E_3)$$

$E_1 \text{ AND } (E_2 \text{ OR } E_3)$	$E_1 \text{ AND } (E_2 \text{ OR } E_3)$
0	1
0	1
0	1
0	1
1	0
1	0
1	0
1	0

Como no se le hace lógica solo se genera 1 si por lo menos el estado activo del canal donde se realiza la función lógica, los otros 0 no son representados

