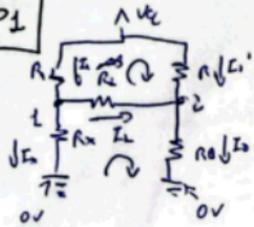


P1



- $U_{CC} = 5V$
- $R_1 = 13 k\Omega$
- $R_2 = 22 k\Omega$
- $R_3 = 0.3 k\Omega$
- $R_L = 100 k\Omega$

$I_L?$

Con. Kirchhoff

~~$I_1 = I_2 + I_3$~~
 ~~$I_L = I_4 = I_0$~~

$$\left. \begin{aligned} I_1 &= I_2 + I_3 \\ I_L + I_1 &= I_0 \end{aligned} \right\} \rightarrow \begin{aligned} \frac{U_{CC} - V_1}{R_1} &= \frac{V_1 - 0}{R_2} + \frac{V_1 - V_2}{R_L} \rightarrow V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_L} \right) - \frac{V_2}{R_L} = \frac{U_{CC}}{R_1} \\ \frac{V_1 - V_2}{R_L} + \frac{U_{CC} - V_2}{R_1} &= \frac{V_2 - 0}{R_0} \rightarrow \frac{V_1}{R_L} + V_2 \left(\frac{1}{R_1} + \frac{1}{R_0} + \frac{1}{R_L} \right) = \frac{U_{CC}}{R_1} \end{aligned}$$

Substitution & algebra

$$\frac{U_{CC}}{R_1} = \frac{5V}{13 k\Omega} = 0.2777 \text{ mA}$$

$$Y_{RL} = 1/100 k\Omega = 0.01 \text{ k}\Omega^{-1}$$

$$\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_L} \right) = \frac{1}{13} + \frac{1}{22} + \frac{1}{100} = 0.046556 \text{ k}\Omega^{-1}$$

$$\left(\frac{1}{R_1} + \frac{1}{R_0} + \frac{1}{R_L} \right) = \frac{1}{13} + \frac{1}{22} + \frac{1}{100} = 0.046556 \text{ k}\Omega^{-1}$$

$$\left. \begin{aligned} 0.046556 \cdot V_1 - 0.01 V_2 &= 0.2777 \\ -0.01 V_1 + 0.0201 V_2 &= 0.2777 \end{aligned} \right\}$$



$$V_1 = 0.60377 V$$

$$V_2 = 0.54577 V$$

$$I_L = \frac{V_1 - V_2}{R_L} = \frac{0.60377 - 0.54577}{100 k\Omega} =$$

$$I_L = 0.6257 \mu A$$

Con Thevenin

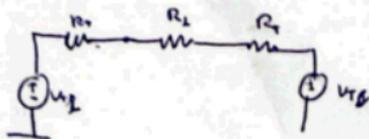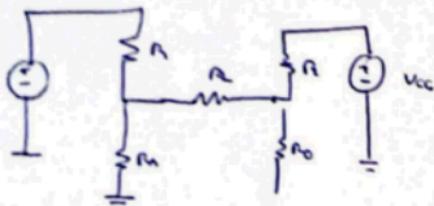

$$V_1 = V_2 \frac{R_2}{R_1 + R_2} = V_{T1}$$

$$V_2 = V_{CC} \frac{R_4}{R_1 + R_4} = V_{T2}$$

$$V_{T1} = \frac{5 \text{ V} \cdot 20 \text{ k}\Omega}{(10 + 20) \text{ k}\Omega} = 0.6667 \text{ V}$$


$$V_{T2} = \frac{5 \text{ V} \cdot 2.2 \text{ k}\Omega}{10 \text{ k}\Omega + 2.2 \text{ k}\Omega} = 0.5455 \text{ V}$$

$$R_{T1} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} = \frac{10 \cdot 20}{10 + 20} = 2.19512 \text{ k}\Omega$$

$$R_{T2} = R_1 \parallel R_4 = \frac{R_1 R_4}{R_1 + R_4} = \frac{10 \cdot 2.2}{10 + 2.2} = 1.96079 \text{ k}\Omega$$

$$I = \frac{V_{T1} - V_{T2}}{R_{T1} + R_2 + R_{T2}} = \frac{0.6667 - 0.5455}{(2.19512 + 10 + 1.96079)} = 0.626 \mu\text{A}$$

P2

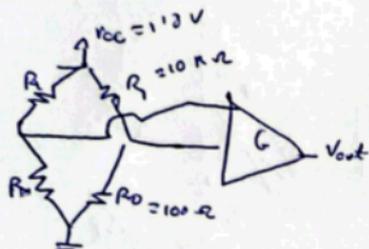

$$R = (100 + 0.17901 \cdot 10^{-3} \cdot 10^3) \Omega \rightarrow$$

$$\theta \in [0, 230^\circ\text{C}]$$

$$P_{R_2} < 10 \text{ mW}$$

$$G \text{ opx } V_o \in [0, 2.5 \text{ V}]$$

$$V_o = G (V_1 - V_2) \quad \mu$$

$$V_1 = V_{CC} \frac{R_4}{R_1 + R_4} \quad \left[V_2 = \frac{V_{CC} + R_0}{R_1 + R_0} = \frac{5\text{V} + 100\Omega}{(10000 + 100)\Omega} = 0.017822 \text{ V} \right]$$

$$R_1 < 0^\circ\text{C} \rightarrow R_1 = 100\Omega \rightarrow V_1 = 0.017822 \text{ V}$$

$$R_1 < 230^\circ\text{C} = 20419\Omega \rightarrow V_1 = \frac{18120419\Omega}{[10000 + 20419]} = 0.03641 \text{ V}$$

$$0.017822 \mu \leq V_1 \leq 0.036411 \checkmark$$

$$\theta = 230^\circ\text{C} \rightarrow V_o = 2.5 = G (0.036411 - 0.017822) \rightarrow G = 136.96$$

*


$$P_{R_2} = V_{R_2} \cdot I_{R_2} = V_1 \cdot \frac{V_1}{R_2} = \frac{V_1^2}{R_2} = \frac{V_{CC}^2 \cdot R_4^2}{(R_1 + R_4)^2 \cdot R_2} = \frac{V_{CC}^2 \cdot R_4}{(R_1 + R_4)^2}$$

substituir g e calcular

$$P_{R_2} = \frac{118^2 \cdot 20419}{(10000 + 20419)^2} = 8.67375 \mu\text{W}$$

No sea equivalente de Norton
Resistencia

P3

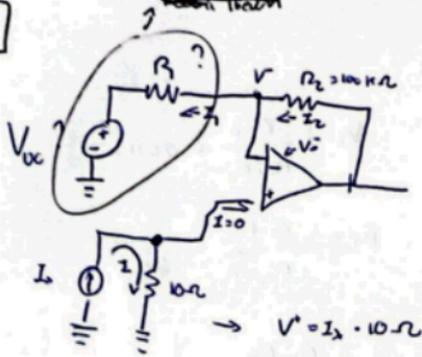

$$4 \text{ mA} \leq I_2 \leq 20 \text{ mA}$$

$$0 \leq V_0 \leq 5 \text{ V}$$

$$V^* = V^-$$

$$I_2 = I_1 \rightarrow \frac{V_0 - V^-}{R_2} = \frac{V^- - V_{oc}}{R_1} \rightarrow \text{Despejamos } V_0$$

$$V_0 = V^- + \frac{R_2}{R_1} (V^- - V_{oc}) = V^- \cdot \left(1 + \frac{R_2}{R_1}\right) - V_{oc} \frac{R_2}{R_1}$$

Substituyendo $V^* = V^- = I_2 \cdot 10 \text{ }\Omega$ en la expresi3n anterior

$$V_0 = I_2 \cdot 10 \text{ }\Omega \left(1 + \frac{R_2}{R_1}\right) - V_{oc} \frac{R_2}{R_1}$$

Aplicamos las condiciones $I_2 = 4 \text{ mA} \rightarrow V_0 = 0$ y $I_2 = 20 \text{ mA}$

$$0 = 4 \text{ mA} \cdot 10 \text{ }\Omega \left(1 + \frac{100 \text{ k}\Omega}{R_1}\right) - V_{oc} \frac{100 \text{ k}\Omega}{R_1}$$


$$0.5 = 20 \text{ mA} \cdot 10 \text{ }\Omega \left(1 + \frac{100 \text{ k}\Omega}{R_1}\right) - V_{oc} \frac{100 \text{ k}\Omega}{R_1}$$

} Solucionamos el sistema de ecuaciones

$$\boxed{R_1 = 3306 \text{ }\Omega}$$

$$\boxed{V_{oc} = 0.0413 \text{ V}}$$

2) Equivalent circuit

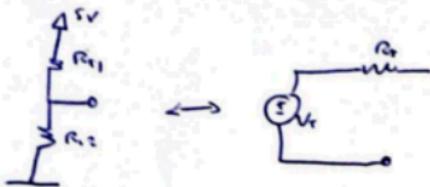

$$V_1 = 5 \frac{R_{L2}}{R_1 + R_{L2}} = 0.0113$$


$$R_{L2} = \frac{R_1 R_{L2}}{R_{L1} + R_{L2}} = 3306$$

0.0113 and 3306

$$\frac{3306}{0.0113} = \frac{\frac{R_{L1} R_{L2}}{R_{L1} + R_{L2}}}{5V \frac{R_{L2}}{R_{L1} + R_{L2}}} = \frac{R_{L1}}{5V}$$

$$R_{L1} = 400.74 \text{ k}\Omega \rightarrow R_{L2} = 3333 \Omega$$

of course ja

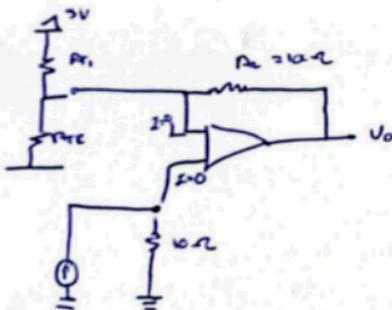

P4

$V_{oc} = 5V$


$500 \Omega < R_x < 1500 \Omega$

$R_1 = 10\,000 \Omega$

$R_2 = 2300 \Omega$

$R_3 = 100\,000 \Omega$

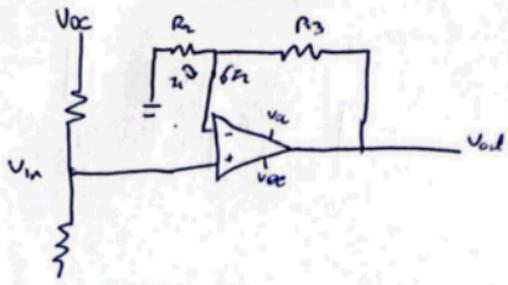- a) $V_{oc} < 10 \text{ V}$
- b) R_x für $V_{out} = 5$
- c) R_x max?



a)
$$\text{Calcul } V_{in} = V_{oc} = \frac{R_x}{R_1 + R_x} \left\{ \begin{array}{l} V_{in \text{ min}} = 5 \cdot \frac{500}{10000 + 500} = 0.2331 \text{ V} \\ V_{in \text{ max}} = 5 \cdot \frac{1500}{10000 + 1500} = 0.2370 \text{ V} \end{array} \right.$$

$I_1 = I_2$

$$\frac{V_{oc} - V_{in}}{R_2} = \frac{V_{in} - V_{out}}{R_3} \rightarrow V_{out} = \frac{R_3}{R_2} V_{in}$$

$$V_{out \text{ min}} = \frac{100000}{2300} = 85034 \text{ V}$$

$$V_{out \text{ max}} = \frac{100000}{2300} = 101103 \text{ V}$$

b) R_x für $V_{out} = 5 \rightarrow V_{in} \rightarrow V_{in} = V_{oc} \frac{R_x}{R_1 + R_x}$

$$V_{in} = \frac{R_2}{R_2} \cdot V_{out} = \frac{2300}{100000} \cdot 5 = 0.114 \text{ V}$$



$$V_{in} = V_{oc} \cdot \frac{R_x}{R_1 + R_x} \rightarrow R_x = \frac{V_{in}(R_1 + R_x)}{V_{oc}} = 5 \cdot \frac{V_{in} R_1 + V_{in} R_x}{V_{oc}} = V_{oc} R_x$$

$$-R_x = V_{in} R_1 = V_{oc} R_x - V_{in} R_x \rightarrow R_x = \frac{V_{in} R_1}{(V_{oc} - V_{in})} = \frac{0.114 \cdot 100000}{(5 - 0.114)} = 233 \Omega$$

$$c) V_{out} = V_{cc} \rightarrow V_m = \frac{2700 \cdot 15}{100000} = 0.42$$

$$R_m = \frac{V_i R_1}{(V_{cc} + V_i)} = \frac{0.42 \cdot 100000}{(5 - 0.42)} = 917.1 \Omega$$

P8

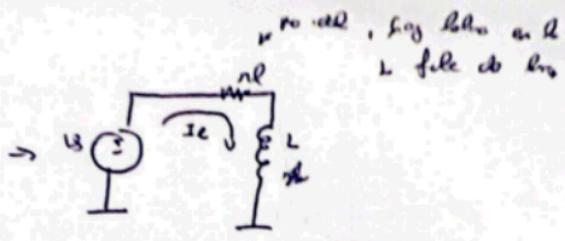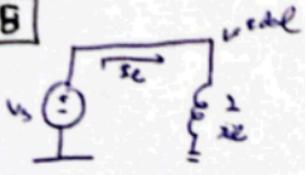

$L = 200 \text{ mH}$ $r_L = 1 \Omega$ $i_L(0) = 0$ $u_s = 12 \text{ V}$ $u_s = 0$

$i_L(\infty)$ $\text{Es } i_L = \frac{u_s}{r_L} = 12 \text{ A}$

Applied Kirchhoff's law $\rightarrow u_s = u_{r_L} + u_L = r_L \cdot i_L + L \cdot \frac{di_L}{dt}$

$i_L(\infty) \rightarrow \frac{u_s}{r_L} = \frac{12}{1} = 12 \text{ A}$

$\frac{u_s}{r_L} = \left(\frac{L}{r_L} \right) \frac{di_L}{dt} + i_L \rightarrow 12 \text{ A} = \tau \frac{di_L}{dt} + i_L$

$i_L(t) = 12 \text{ A} (1 - e^{-t/\tau})$ $\tau = \frac{0.2 \text{ H}}{1} = 0.2 \text{ s}$

0.93 means 93% of the current value is reached

$0.93 \cdot 12 \text{ A} = 12 \text{ A} (1 - e^{-t/0.2}) \rightarrow e^{-t/0.2} = 0.07$


$e^{-t/0.2} = 0.07 \rightarrow t = -0.2 \ln(0.07) \approx 0.93 \text{ s} = t$

$P_{\text{max}} = I_L^2 r_L = 12^2 \cdot 1 = 144 \text{ W}$

PG

Abse $\epsilon [0, t_p]$ $\rightarrow t_p = 10 \text{ ms}$, so uoc dolo 10 ms \rightarrow uoc \rightarrow uoc \rightarrow uoc
 dolo dolo 10 ms \rightarrow uoc \rightarrow uoc

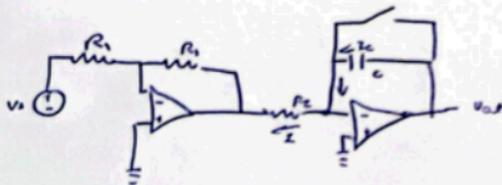$V_s = 1 \text{ V}$
 $R_1 = 10 \text{ k}\Omega$
 $C = 100 \text{ nF}$



$$\frac{V_s - 0}{R_1} = \frac{0 - V_1}{R_1} \rightarrow V_1 = -V_s ; V_1 = -1 \text{ V}$$

$$\rightarrow S_1 \rightarrow \text{cuk cod} \rightarrow V_0 = V^- \rightarrow V_0 = 0 \text{ V} \rightarrow V_C = 0$$

$$\rightarrow S_1 \rightarrow \text{dolo dolo} \rightarrow I_C = I \rightarrow I = \frac{0 - V_1}{R_2} = \frac{1}{10} = 0.1 \text{ mA}$$


$$I_C = C \cdot \frac{dV_C}{dt} = 0.1 \text{ mA}$$

$$\frac{dV_C}{dt} = \frac{0.1}{C} ; \int_0^{V_C(t)} dV_C = \frac{1}{C} \cdot \int_0^t 0.1 \text{ mA} dt$$

$$V_C(t) = \frac{10^{-4}}{100 \cdot 10^{-9}} \cdot t = 10^3 \frac{\text{V}}{\text{s}} \cdot t$$

$$t = t_p = 10 \text{ ms}$$


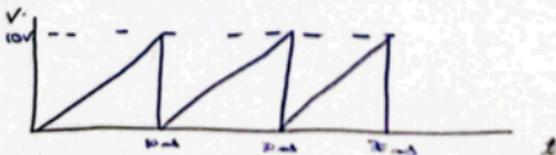
$$\rightarrow V_C(t) = 10^3 \cdot 10 \cdot 10^{-3} = 10 \text{ V}$$



P7

$R = 10 \text{ k}\Omega$
 $R_2 = 47 \text{ k}\Omega$
 $C = 22 \text{ nF}$

Vo a fun de Vi?
 O que de Oble?

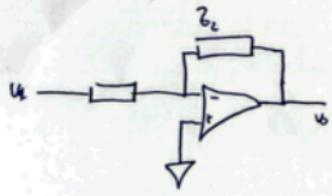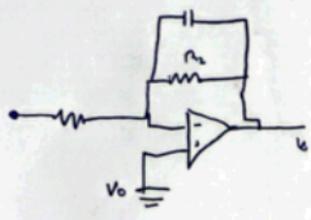


$$\frac{1}{Z_f} = \frac{1}{R_2} + \frac{1}{j\omega C} = \frac{1}{R_2} + j\omega C =$$

$$Z_f = R_2 \parallel \left(\frac{1}{j\omega C} \right) = \frac{R_2 \cdot \frac{1}{j\omega C}}{R_2 + \frac{1}{j\omega C}} = \frac{R_2}{j\omega C R_2 + 1}$$

$V^+ = 0 \rightarrow V^- = 0$

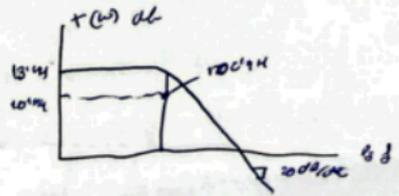$I_1 = I_2 \Rightarrow \frac{V_i - 0}{R} = \frac{0 - V_o}{Z_f} \Rightarrow \frac{V_i}{R} = -\frac{V_o}{Z_f}$




Secon $T(j\omega)$ $\Rightarrow T(j\omega) = \frac{V_o}{V_i} = -\frac{Z_f}{R} = -\frac{R_2}{R(j\omega C R_2 + 1)} = \frac{-R_2/R_1}{1 + j\omega R_2 C}$

$R_2/R_1 = 4.7$
 $\omega_{corte} = 10^4$

$R_2 C = 47 \cdot 10^3 \cdot 22 \cdot 10^{-9} \text{ F} = 1.034 \mu\text{s}$

$\omega_{RC} = 2\pi f = R_2 C = f/f_c$

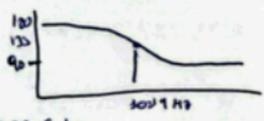$f_c = \frac{1}{2\pi R_2 C} = \frac{1}{2\pi \cdot 1.034 \mu\text{s}} = 102.6 \text{ kHz}$



$T\omega = \frac{R_2}{R \sqrt{1 + (\omega R_2 C)^2}} \cdot \frac{180 - \tan^{-1}(\omega R_2 C)}$

fase de 180 graus que al no reglo en -180 e mais
 a do decimador

3. $f \rightarrow 0 \Rightarrow T(\omega) = |T_0| \angle 180^\circ$

3. $f \rightarrow \infty \Rightarrow \frac{|T_0|}{\sqrt{2}} \angle 135 - 90^\circ$ 3. $f \rightarrow \infty \rightarrow \frac{T_0}{\sqrt{2}} \angle 130 - 45^\circ$